

Intuitive Analog Circuit Design

Intuitive Analog Circuit Design

*A Problem-Solving Approach
using Design Case Studies*

By

Marc T. Thompson, Ph.D.



ELSEVIER

AMSTERDAM • BOSTON • HEIDELBERG • LONDON
NEW YORK • OXFORD • PARIS • SAN DIEGO
SAN FRANCISCO • SINGAPORE • SYDNEY • TOKYO

Newnes is an imprint of Elsevier



Newnes

Newnes is an imprint of Elsevier
30 Corporate Drive, Suite 400, Burlington, MA 01803, USA
Linacre House, Jordan Hill, Oxford OX2 8DP, UK

Copyright © 2006, Elsevier Inc. All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior written permission of the publisher.

Permissions may be sought directly from Elsevier's Science & Technology Rights Department in Oxford, UK: phone: (+44) 1865 843830, fax: (+44) 1865 853333, e-mail: permissions@elsevier.com.uk. You may also complete your request on-line via the Elsevier homepage (<http://elsevier.com>), by selecting "Customer Support" and then "Obtaining Permissions."



Recognizing the importance of preserving what has been written,
Elsevier prints its books on acid-free paper whenever possible.

Library of Congress Cataloging-in-Publication Data

Thompson, Marc T.

Intuitive analog circuit design.

p. cm.

ISBN-13: 978-0-7506-7786-8 (pbk. : alk. paper)

ISBN-10: 0-7506-7786-4 (pbk. : alk. paper) 1. Electronic circuit design.

I. Title.

TK7867.T48165 2006

621.3815--dc22

2005036750

British Library Cataloguing-in-Publication Data

A catalogue record for this book is available from the British Library.

ISBN-13: 978-0-7506-7786-8

ISBN-10: 0-7506-7786-4

For information on all Newnes publications
visit our Web site at www.books.elsevier.com

06 07 08 09 10 10 9 8 7 6 5 4 3 2 1

Printed in the United States of America

Working together to grow
libraries in developing countries

www.elsevier.com | www.bookaid.org | www.sabre.org

ELSEVIER

BOOK AID
International

Sabre Foundation

In memoriam

To my mother, Minnie Ann Thompson,
who bought me my first transistors when I was a child.

Dedication

To Lisa and Sophie M., for your love and patience.
The book is finally done. Mazel tov!

Contents

Preface	<i>x</i>
Chapter 1: Introduction and Motivation	1
The Need for Analog Designers.....	1
Some Early History of Technological Advances in Analog Integrated Circuits	2
Digital vs. Analog Implementation: Designer's Choice	6
So, Why Do We Become Analog Designers?	8
Note on Nomenclature in this Text	9
Note on Coverage in this Book.....	9
References.....	10
U.S. Patents.....	12
Chapter 2: Review of Signal-Processing Basics.....	13
Review of Laplace Transforms, Transfer Functions and Pole-Zero Plots	13
First-Order System Response	15
Second-Order Systems.....	23
Review of Resonant Electrical Circuits	33
Use of Energy Methods to Analyze Undamped Resonant Circuits	34
Transfer Functions, Pole/Zero Plots and Bode Plots	36
Risetime for Cascaded Systems	37
Chapter 2 Problems.....	38
References.....	42
Chapter 3: Review of Diode Physics and the Ideal (and Later, Nonideal) Diode.....	43
Current Flow in Insulators, Good Conductors and Semiconductors	43
Electrons and Holes	45
Drift, Diffusion, Recombination and Generation.....	48
Effects of Semiconductor Doping.....	53
PN Junction Under Thermal Equilibrium	54
PN Junction Under Applied Forward Bias.....	57

Contents

Reverse Biased Diode	61
Ideal Diode Equation	62
Charge Storage in Diodes	63
Charge Storage in the Diode Under Forward Bias	65
Reverse Recovery in Bipolar Diodes	65
Reverse Breakdown	66
Taking a Look at a Diode Datasheet	67
Some Quick Comments on Schottky Diodes	70
Chapter 3 Problems	71
References	74
Chapter 4: Bipolar Transistor Models	75
A Little Bit of History	75
Basic NPN Transistor	76
Transistor Models in Different Operating Regions	79
Low-Frequency Incremental Bipolar Transistor Model	82
High-Frequency Incremental Model	85
Reading a Transistor Datasheet	88
Limitations of Hybrid-Pi Model	93
Chapter 4 Problems	94
References	95
Chapter 5: Basic Bipolar Transistor Amplifiers and Biasing	97
The Issue of Transistor Biasing	97
Some Transistor Amplifiers	101
Chapter 5 Problems	121
References	125
Chapter 6: Bandwidth Estimation Techniques and the Method of Open-Circuit Time Constants	127
Introduction to Open-Circuit Time Constants	127
Transistor Amplifier Examples	132
Chapter 6 Problems	156
References	159
Chapter 7: Advanced Transistor Amplifier Techniques	161
Worst-Case Open-Circuit Time Constant Calculations	161
High-Frequency Output and Input Impedance of Emitter-Follower Buffers	168
Bootstrapping	177
Short-Circuit Time Constants	184

Pole Splitting.....	196
Chapter 7 Problems.....	202
References.....	205
Chapter 8: High-Gain Bipolar Amplifiers and BJT Current Mirrors	207
The Need to Augment the Hybrid-Pi Model.....	207
Base-Width Modulation.....	209
Finding Parameters from a Transistor Datasheet.....	211
Common-Emitter Amplifier with Current Source Load.....	212
Building Blocks.....	213
Chapter 8 Problems.....	238
References.....	240
Chapter 9: Introduction to MOSFET Devices and	
Basic MOS Amplifiers	241
Some Early History of Field-Effect Transistors.....	241
Qualitative Discussion of Basic MOS Devices.....	242
Figuring Out the V/I Curve of a MOS Device.....	243
MOS Small-Signal Model (Low Frequency).....	246
MOS Small-Signal Model (High Frequency).....	247
Basic MOS Amplifiers.....	248
Chapter 9 Problems.....	266
References.....	268
Chapter 10: Bipolar Transistor Switching and the	
Charge Control Model.....	269
Introduction.....	269
Development of the Switching Models.....	269
Reverse-Active Region.....	271
Saturation.....	272
Junction Capacitances.....	274
Relationship Between Charge Control and Hybrid-Pi Parameters.....	274
Finding Junction Capacitances from the Datasheet.....	275
Manufacturers' Testing.....	277
Charge Control Model Examples.....	277
Emitter Switching.....	292
2N2222 Datasheet Excerpts.....	294
Chapter 10 Problems.....	298
References.....	303

Chapter 11: Review of Feedback Systems.....	305
Introduction and Some Early History of Feedback Control	305
Invention of the Negative Feedback Amplifier	306
Control System Basics	308
Loop Transmission and Disturbance Rejection	309
Stability	310
Routh Stability Criterion.....	311
The Phase Margin and Gain Margin Tests	314
Relationship Between Damping Ratio and Phase Margin.....	315
Loop Compensation Techniques—Lead and Lag Networks	316
Parenthetical Comment on Some Interesting Feedback Loops	317
Appendix: MATLAB Scripts	338
Chapter 11 Problems.....	342
References.....	345
Chapter 12: Basic Operational Amplifier Topologies and a Case Study	347
Basic Device Operation	347
Brief Review of LM741 Op-Amp Schematic	358
Some Real-World Limitations of Operational Amplifiers	359
Chapter 12 Problems.....	366
References.....	367
Chapter 13: Review of Current Feedback Operational Amplifiers	369
Conventional Voltage-Feedback Op-Amp and the Constant “Gain Bandwidth Product” Paradigm.....	369
Slew Rate Limitations in Conventional Op-Amps.....	371
Basic Current Feedback Op-Amp.....	372
Absence of Slew Rate Limit in Current Feedback Op-Amps.....	375
Manufacturer’s Datasheet Information for a Current Feedback Amplifier	379
A More Detailed Model and Some Comments on Current-Feedback Op-Amp Limitations.....	381
Chapter 13 Problems.....	382
References.....	383
Chapter 14: Analog Low-Pass Filters.....	385
Introduction.....	385
Review of Low-Pass Filter Basics	386
Butterworth Filter.....	387
Chebyshev Filter	390

Bessel Filter	395
Comparison of Responses of Different Filter Types.....	398
Filter Implementation.....	400
Chapter 14 Problems.....	414
References.....	416
Chapter 15: Review of Passive Components and a Case Study in PC Board Layout.....	417
Resistors.....	417
Comments on Surface-Mount Resistors	419
Comments on Resistor Types.....	420
Capacitors	421
Inductors	424
Discussion of Printed-Circuit Board Layout Issues.....	425
Approximate Inductance of a PC Board Trace Above a Ground Plane	428
Chapter 15 Problems.....	436
References.....	437
Chapter 16: Other Useful Design Techniques and Loose Ends	439
Thermal Circuits	439
Steady-State Model of Conductive Heat Transfer	440
Thermal Energy Storage	441
Using Thermal Circuit Analogies to Determine Static Semiconductor Junction Temperature.....	444
Mechanical Circuit Analogies.....	444
The Translinear Principle.....	449
Input Impedance of Infinitely Long Resistive Ladder	451
Transmission Lines 101	451
Node Equations and Cramer's Rule.....	455
Finding Oscillation Modes.....	458
Some Comments on Scaling Laws in Nature	463
Chapter 16 Problems.....	469
References.....	472
Index	475
What's on the CD-ROM?.....	480

Preface

What? Another textbook on analog circuit design? Well, this is not a textbook *per se*; rather, it is designed to be more of a design handbook for practicing engineers and students interested in learning more real-world techniques for designing and analyzing analog circuits using transistors, diodes, and operational amplifiers. The hope is that the reader will find a good mixture of theoretical techniques and also real-world design examples and test results.

This author is a practicing electrical engineer in the analog and power electronics realm who also has had the opportunity to teach at Worcester Polytechnic Institute.

The careful reader, upon review of the chapter references, will note that I have a fondness for using older references. This is due in part to the fact that the authors of these older texts and papers did not have computers available to them for circuit simulations and mathematical number-crunching. These references, in many cases, give very useful approximations, intuitive insights, and different ways of looking at difficult circuit analysis problems.

Intended Audience

This text is loosely based on a set of course notes designed for my graduate-level analog circuit design seminar offered at Worcester Polytechnic Institute. Students who take my course have already taken undergraduate-level courses covering transistors, signal processing, Bode plots and the like. Furthermore, it is the author's hope that the techniques shown in the book will be useful for practicing analog (and perhaps even *digital!*) design engineers.

Text Outline

Chapters 1 and 2 offer introductory material. Chapter 1 serves as an introduction and motivation to analog circuit design in general, with selected history thrown into the mix. Chapter 2 covers important signal-processing concepts that are used in later chapters, so that the reader will be on the "same page" as the author.

Chapters 3 to 8 cover the bipolar device physics, the bipolar junction transistor (BJT), transistor amplifiers, and approximation techniques for bandwidth estimation and switching speed analysis.

Chapter 9 covers the basics of CMOS and CMOS amplifiers. The bandwidth estimation techniques developed in earlier chapters for amplifier design work well for CMOS devices as well.

Preface

Chapter 10 covers transistor switching. How do you get a transistor to turn ON and OFF quickly, and how do you estimate that speed?

Chapter 11 is a review of feedback systems and of the Bode plot/phase margin method of designing stable feedback systems.

Chapters 12–13 cover the design, use and limitations of real-world operational amplifiers, including voltage-feedback and current-feedback op-amps.

Chapter 14 covers the basics of analog low-pass filter design, including ladder and active implementations of Butterworth, Chebyshev, elliptic and Bessel filters.

Chapter 15 covers real-world design issues such as PC board layout rules-of-thumb and the use and limitations of passive components.

Chapter 16 is a potpourri of useful design techniques and tricks that don't fit into the other chapters.

Throughout the text, some illustrative analysis problems and MATLAB® and PSPICE design examples are haphazardly sprinkled.

Acknowledgments

The author would like to acknowledge the learned professors and teaching assistants at the Massachusetts Institute of Technology who taught him many of the techniques shown in this book. They include Prof. Jim Roberge, Prof. Bill Siebert, Prof. Bill Peake, Prof. Marty Schlecht, Leo Casey, Tom Lee, Prof. Harry Lee, Prof. Campbell Searle, Prof. Amar Bose, and Prof. Dick Thornton.

This text has evolved from courses the author taught over the past years at Worcester Polytechnic Institute. Therefore, further thanks go to W.P.I. and its students and faculty who directly and indirectly contributed to this text. The author also acknowledges the indirect contributions of his W.P.I. students who, through their probing questions and careful reading of the course notes, have identified numerous typographical errors and half-truths, which hopefully have been fully expunged from this edition.

The author gratefully acknowledges the patience and technical support provided by the staff at Elsevier. The author also wishes to thank my friend and colleague Dr. Alexander Kusko, who reviewed the manuscript and offered many useful suggestions. Also thanks to my friend Dr. Jeff Roblee, who read the manuscript from a mechanical engineering point-of-view and offered many useful suggestions.

Plots were created using MATLAB and the Microsim Student Version of PSPICE, version 8.0.

Marc T. Thompson
Harvard Labs
Harvard, Massachusetts
October, 2005