



Power Quality

Notes 2-1 (MT)

Marc Thompson, Ph.D.
Senior Managing Engineer
Exponent
21 Strathmore Road
Natick, MA 01760

Alex Kusko, Sc.D, P.E.
Vice President
Exponent
21 Strathmore Road
Natick, MA 01760

Adjunct Associate Professor of Electrical
Engineering
Worcester Polytechnic Institute
Worcester, MA 01609

Class #2 - Hour #1 (4/12/05)


Harmonic Current Sources

- Some more definitions
 - Crest factor
 - THD
- Single-phase rectifiers
 - Inductor filter
 - Capacitor filter
- Three-phase rectifiers
 - Inductor filter
 - Harmonics


Crest Factor

- Ratio of peak value to RMS value
- For a sinewave, crest factor = 1.4
 - Peak = 1; RMS = 0.707
- For a square wave, crest factor = 1
 - Peak = 1; RMS = 1


Harmonics and THD - Sinewave

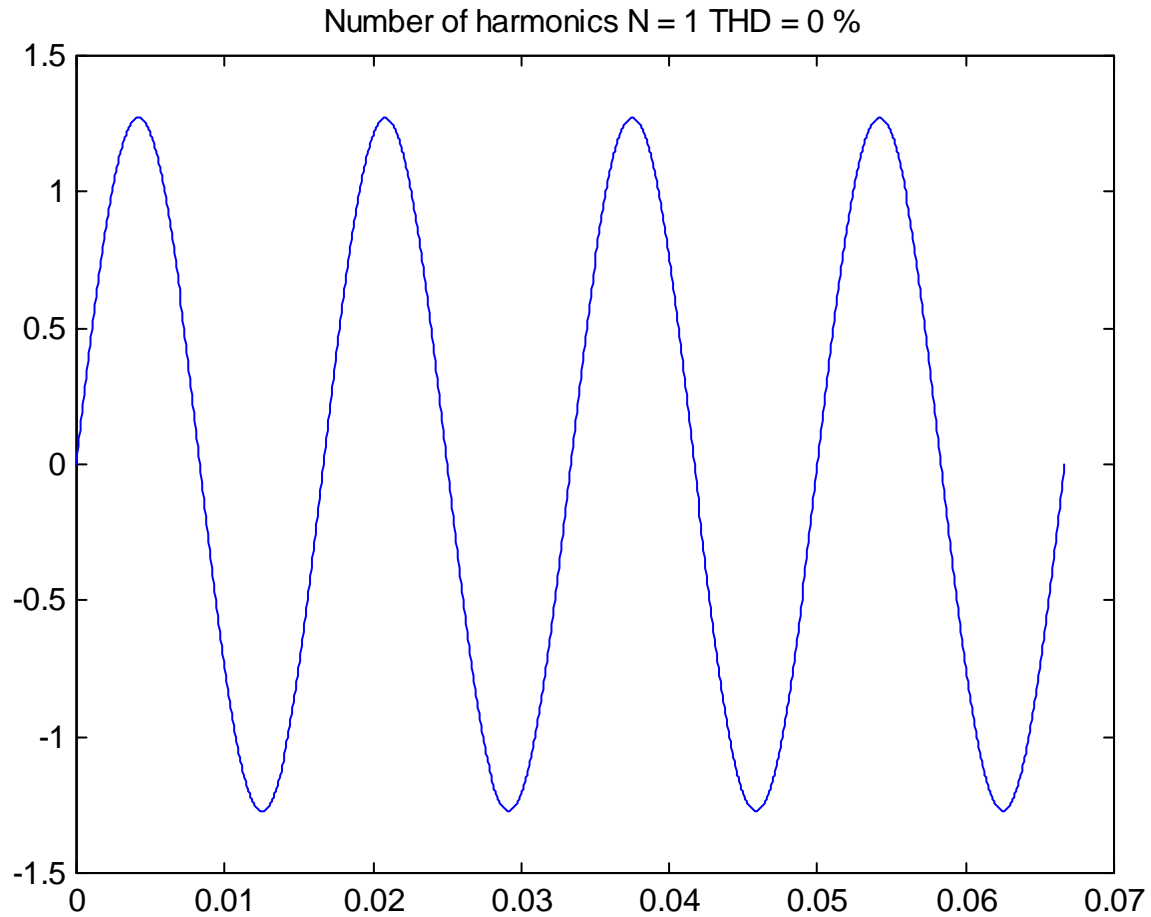

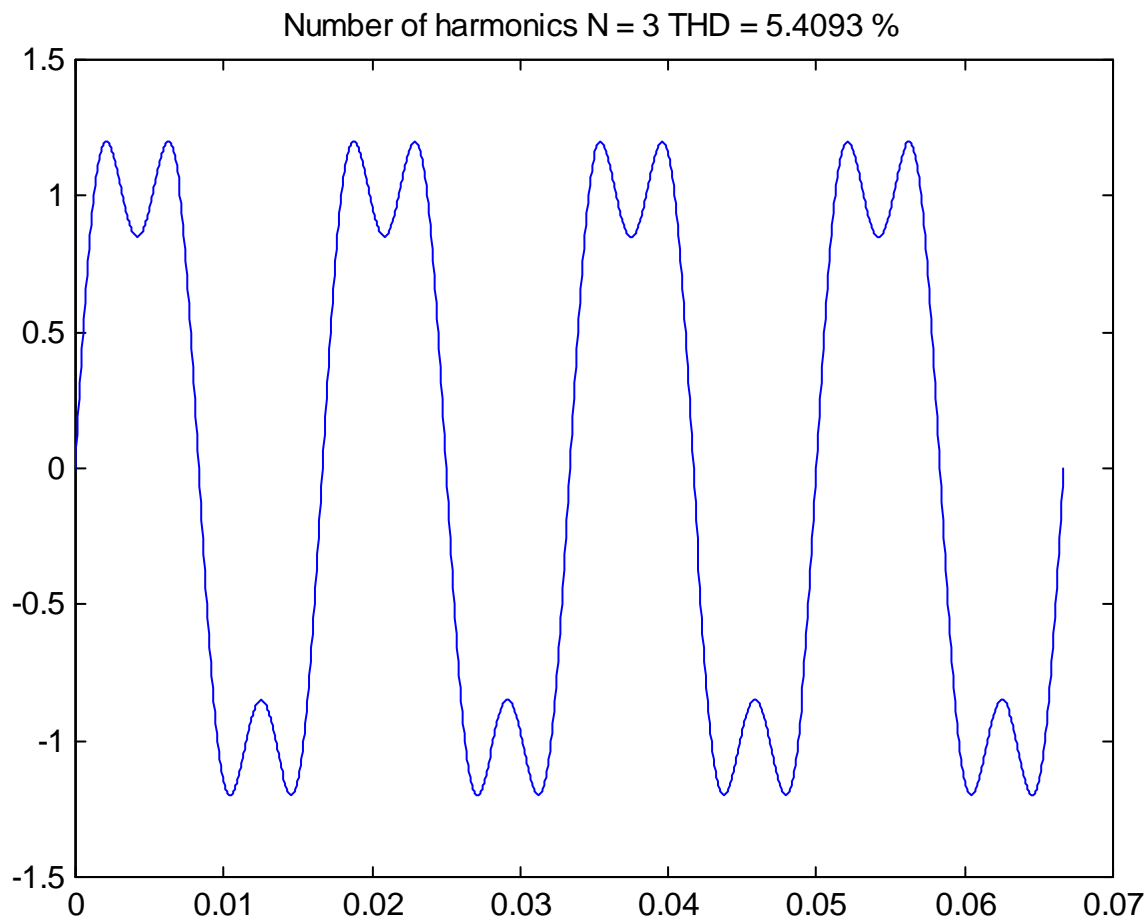
Harmonics and THD - Sinewave + 3rd Harmonic



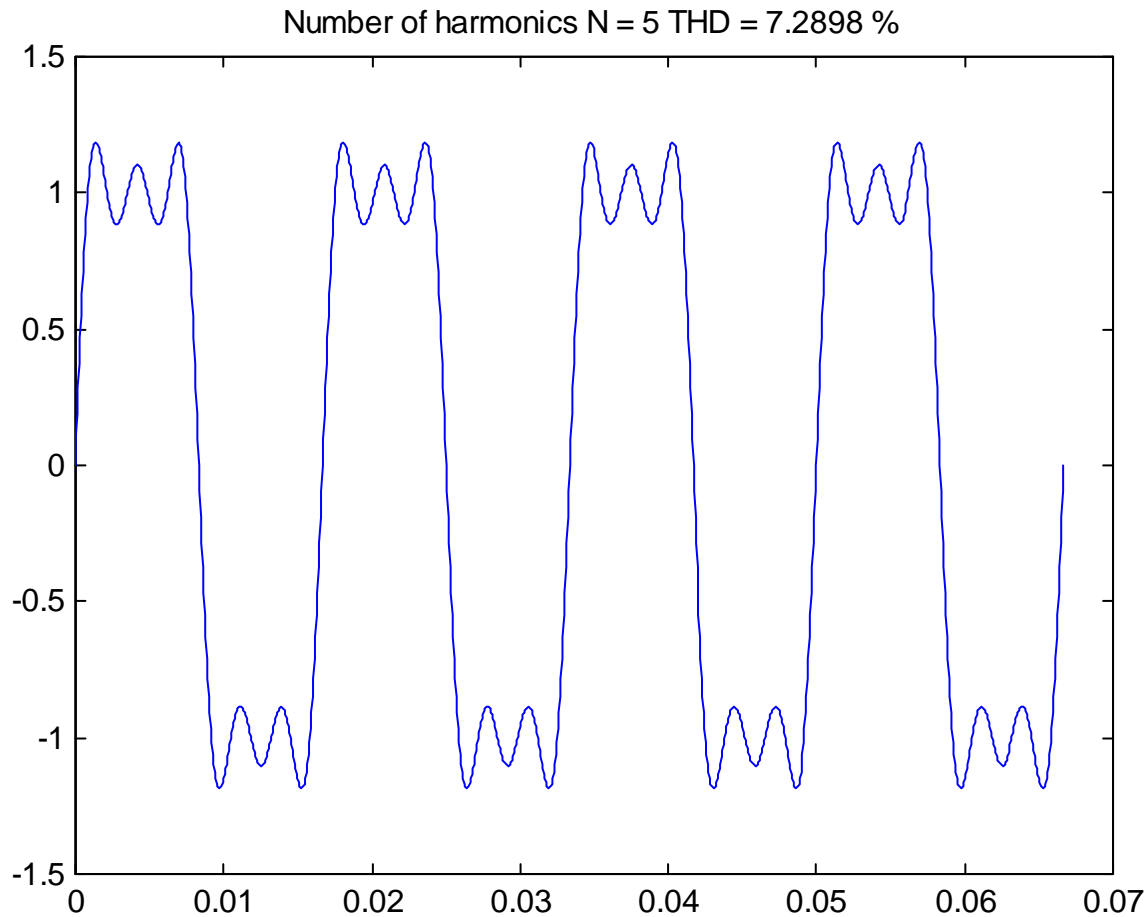Harmonics and THD --- Sinewave + 3rd + 5th Harmonic




Harmonics and THD - Up to N = 103

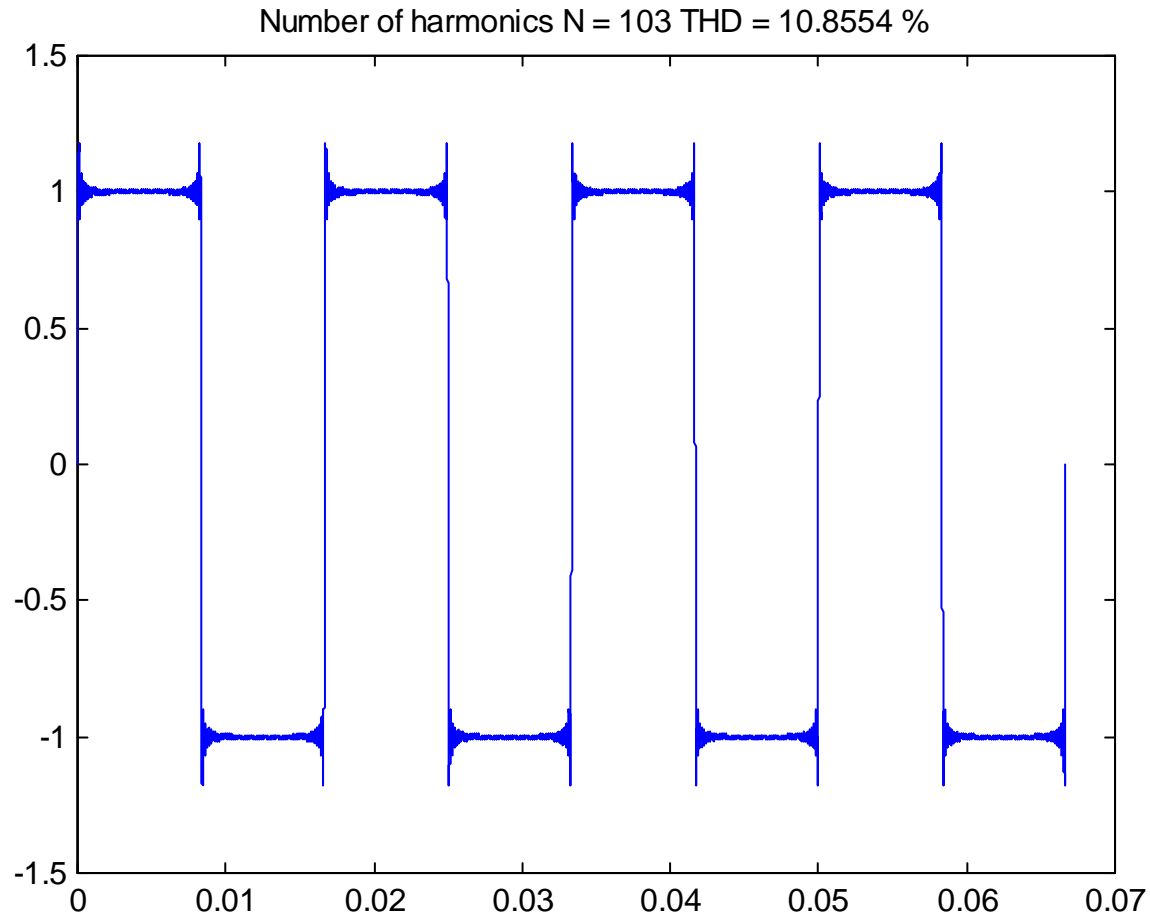

Half-Wave Rectifier, Resistive Load

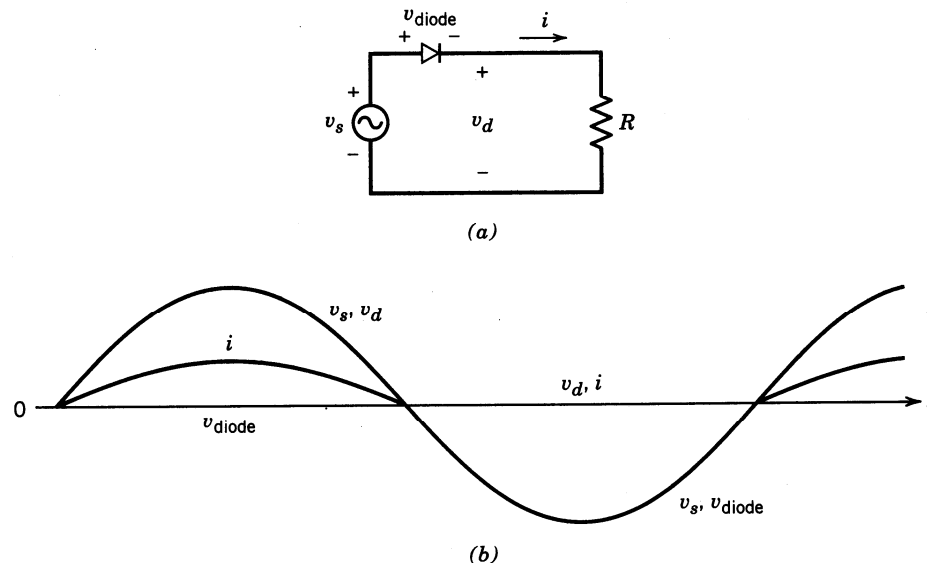- Simplest, cheapest rectifier
- Line current has DC component; this current appears in neutral
- High harmonic content, Power factor = 0.7




$$P.F. = \frac{P_{avg}}{V_{RMS} I_{RMS}}$$

Figure 5-2 Basic rectifier with a load resistance.


Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 80

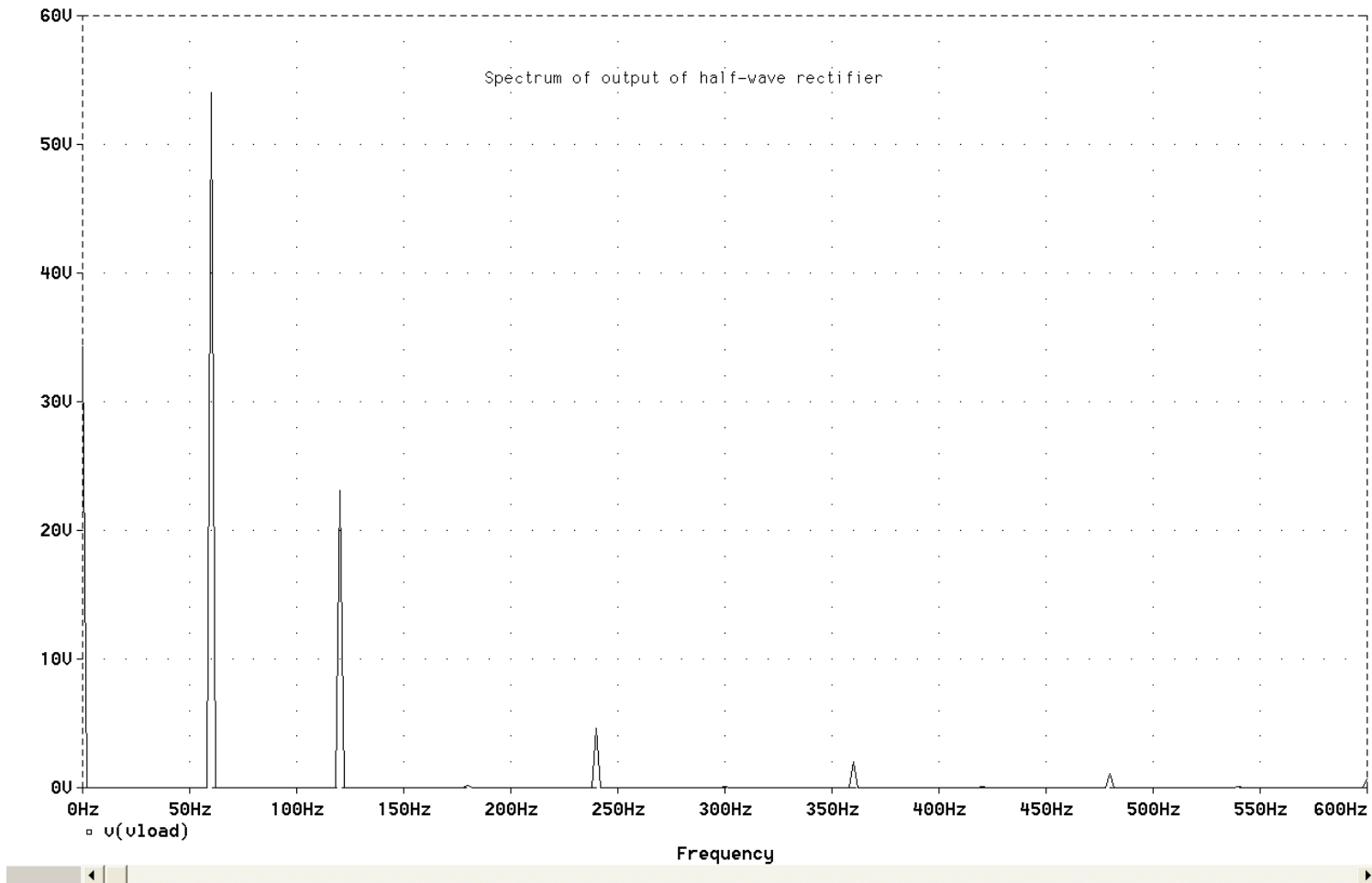Half-Wave Rectifier, Resistive Load --- Spectrum of Load Voltage




Half Wave Rectifier with RC Load

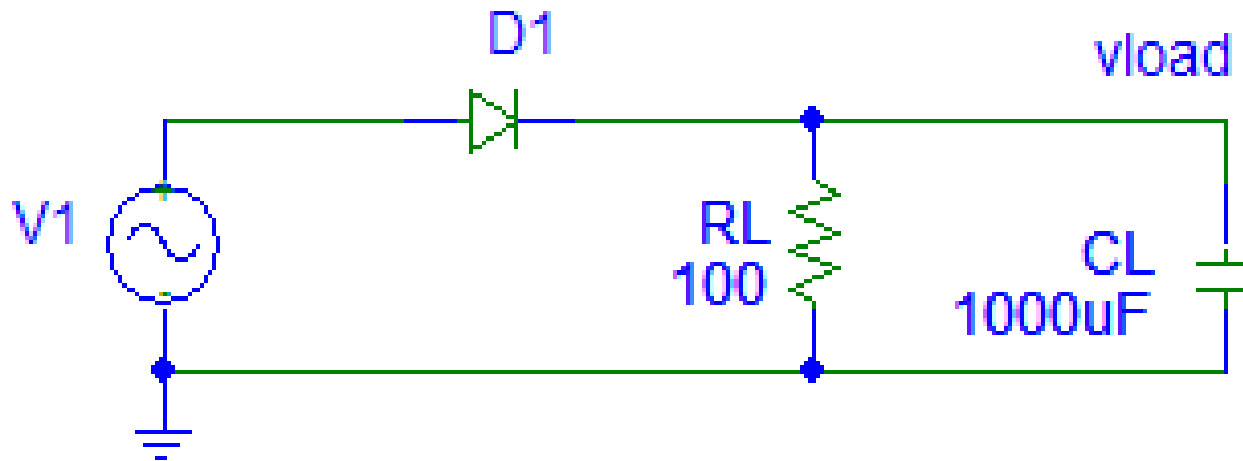- More practical rectifier
- For large RC, this behaves like a peak detector




Half Wave Rectifier with RC Load

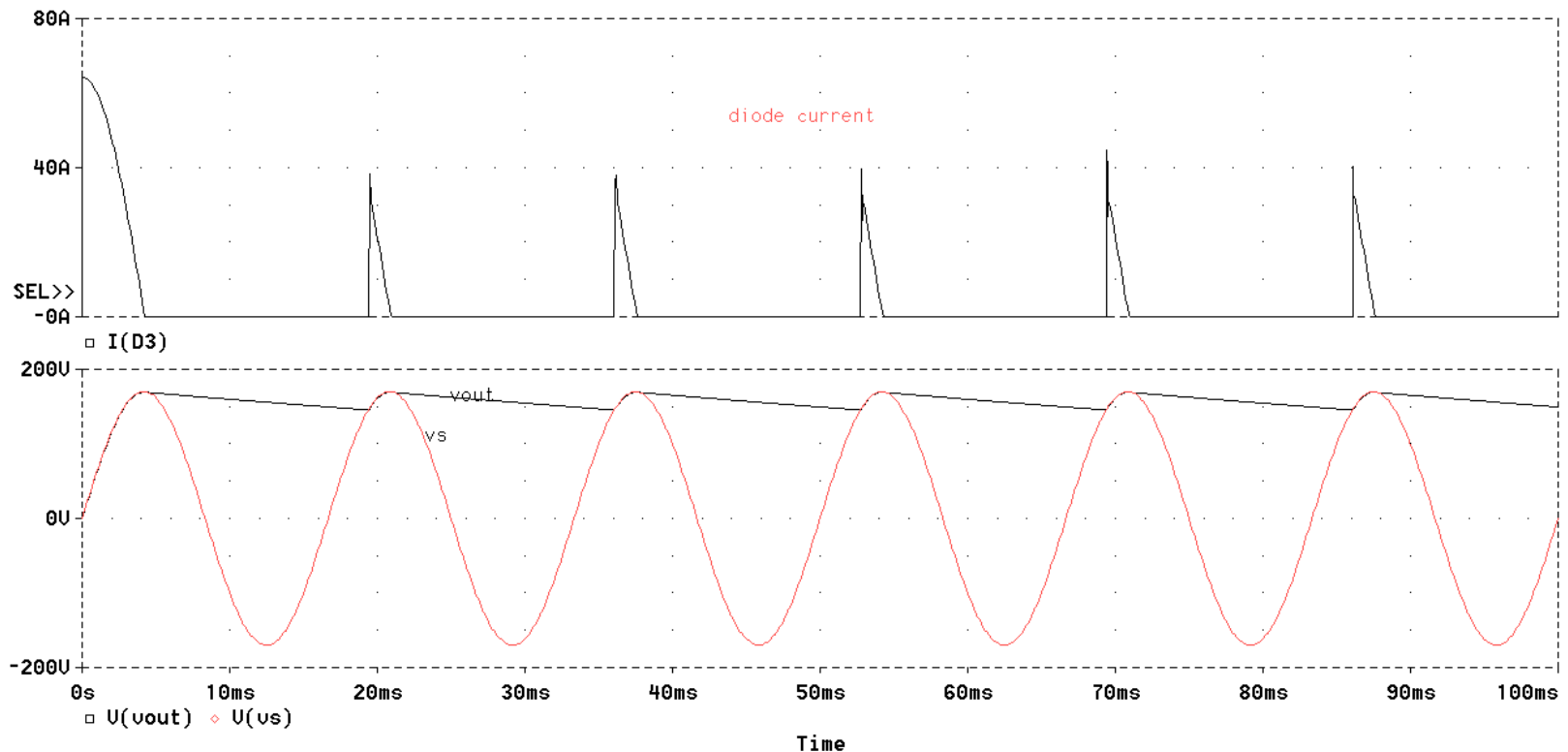- Note poor power factor due to peaky line current
- Note DC component of line current



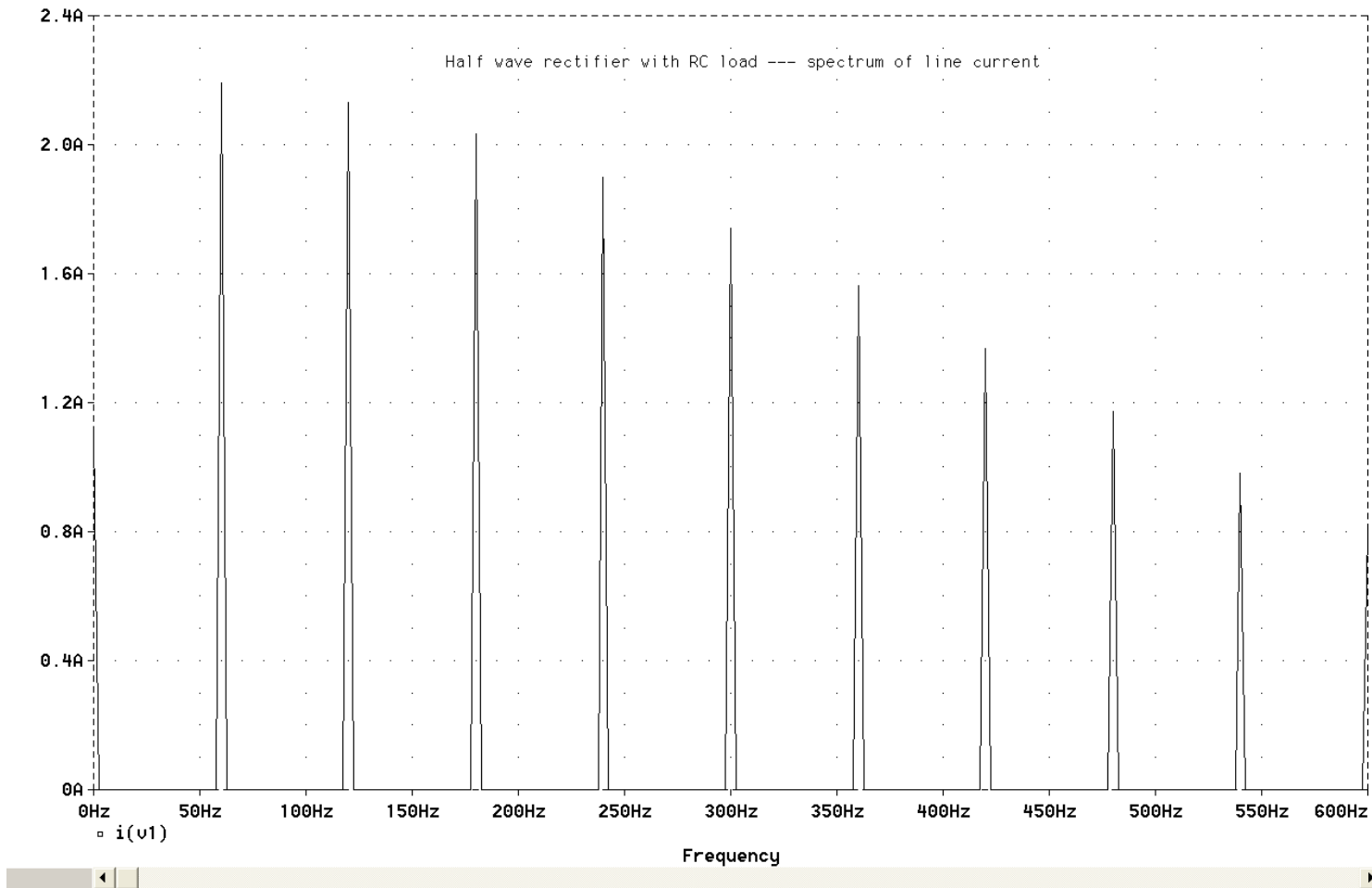Half Wave Rectifier with RC Load --- Spectrum of Line Current



Single-Phase Full-Wave Rectifier

- Large capacitor at the dc output for filtering and energy storage
- L_s models inductance of power line

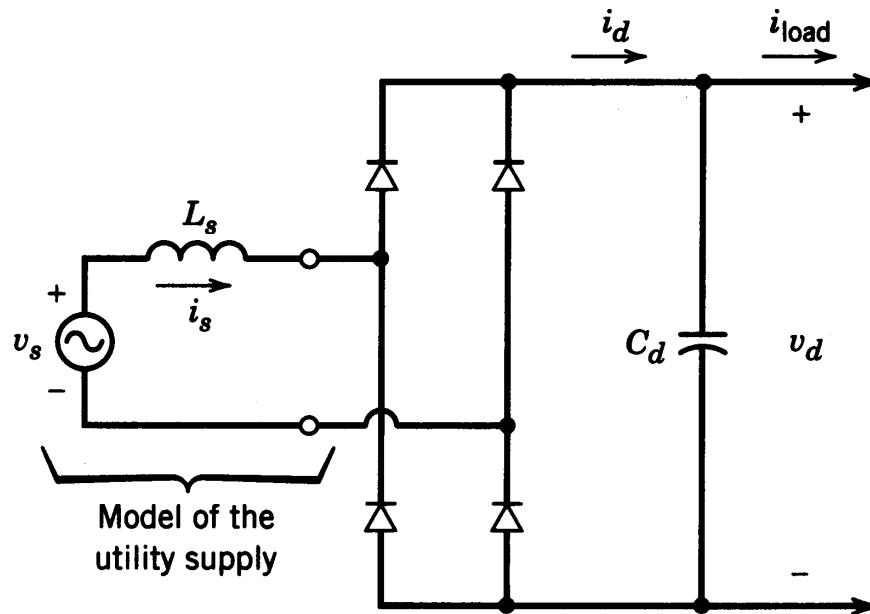


Figure 5-5 Single-phase diode bridge rectifier.

Comments on Line Impedance

- Very roughly, line inductance is ~ 1 microHenry per meter of wire length
 - We can calculate this in closed form for parallel-wire line, or for circular loop of round wire
- Wire DC resistance can be found from wire chart. E.g., #14 AWG is approximately $0.01\Omega/\text{meter}$ at 75C

Full-Wave Diode Rectifier Analysis

- Two simple (idealized) cases to begin with
- Resistor load models unity power factor load
- I_d load models large inductive load


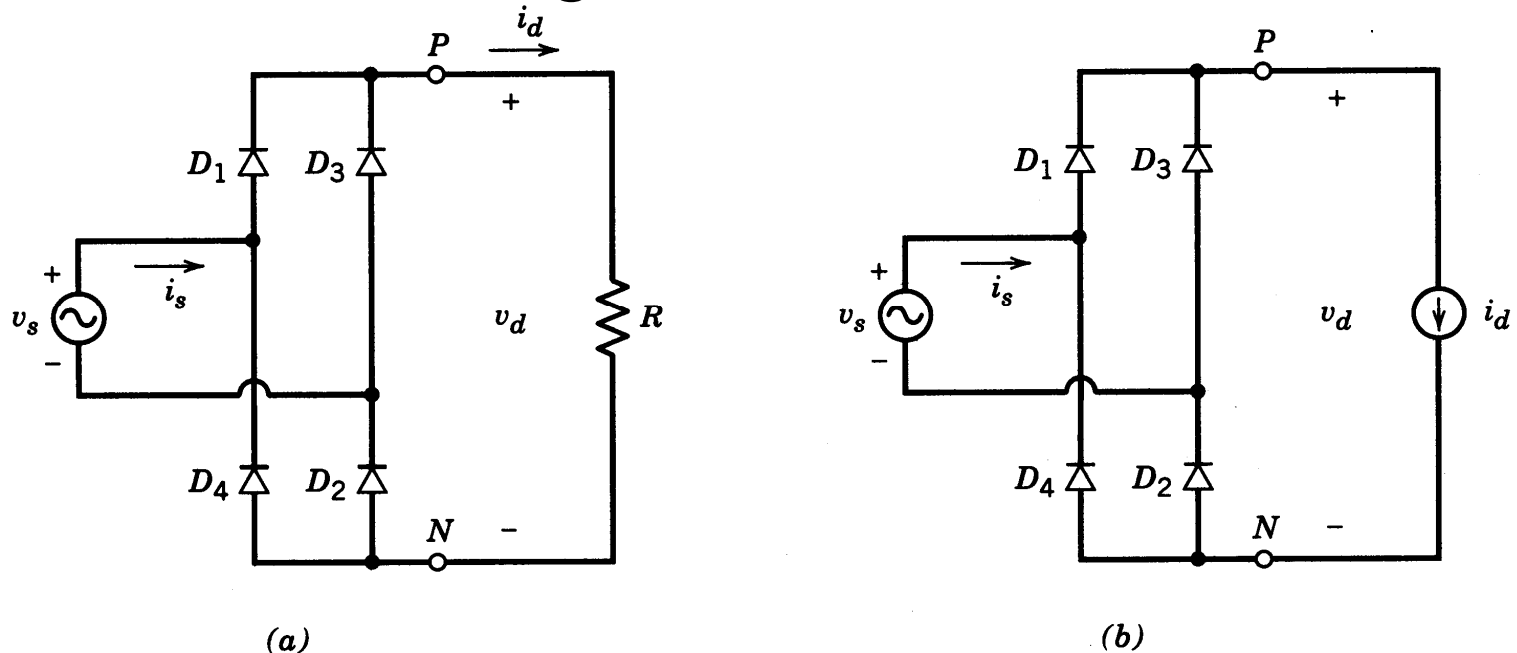
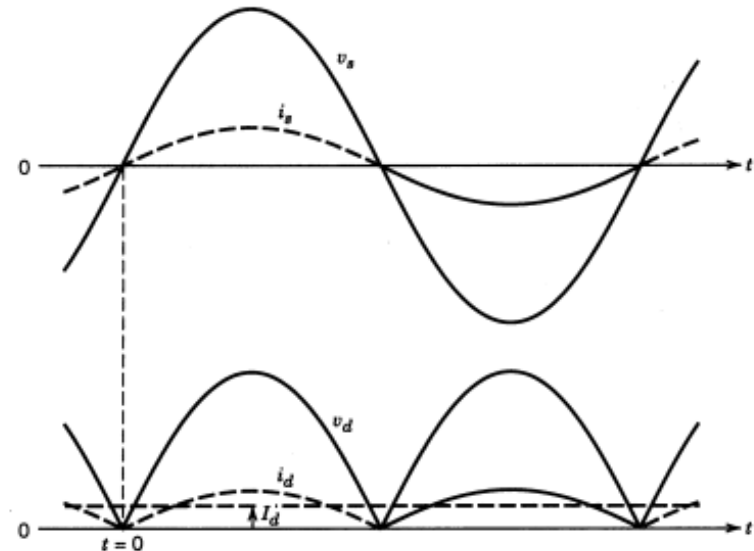


Figure 5-6 Idealized diode bridge rectifiers with $L_s = 0$.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 84

Diode-Rectifier Bridge Waveforms with Resistive Load

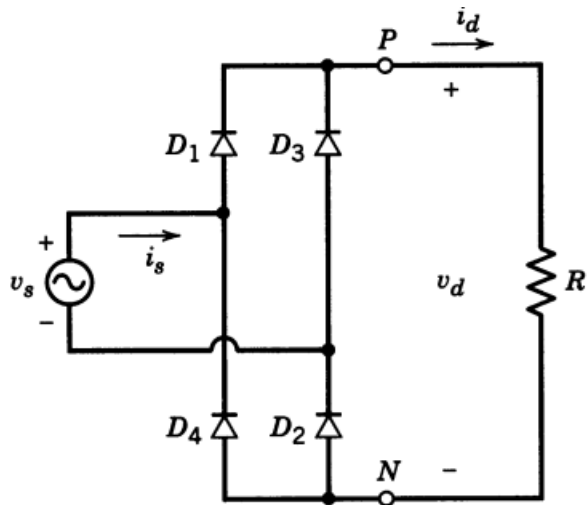
- Resistive load models high power factor load
- Note that the line current is in phase and has same shape as line voltage; hence $PF = 1$



Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 84-85


Single-Phase Full Wave Rectifier Bridge

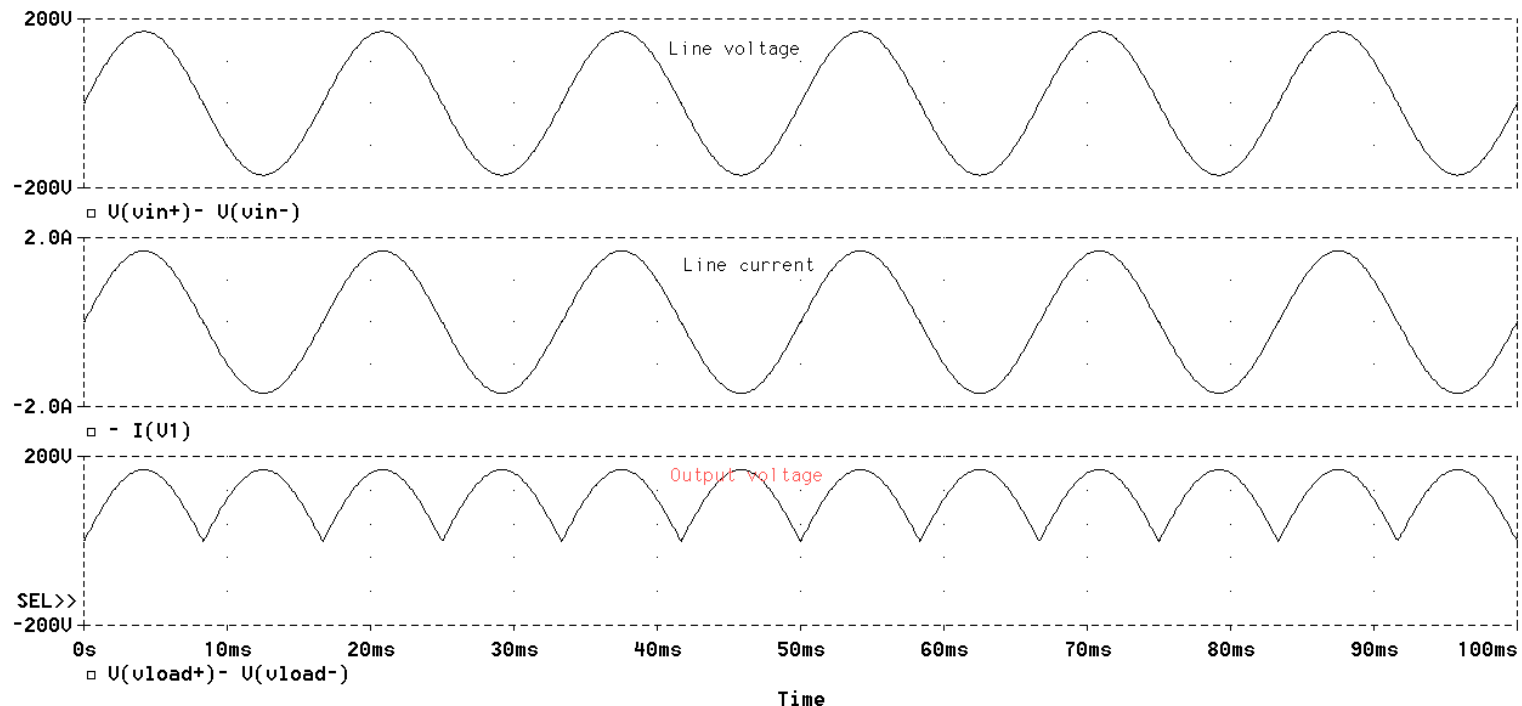- Only 2 diodes are on at any time
- Power factor = 1 (ignoring diode drops)
- Average value of output is 2x that of HWR



Diode-Rectifier Bridge Waveforms --- Large Inductive (~ Current Source) Load

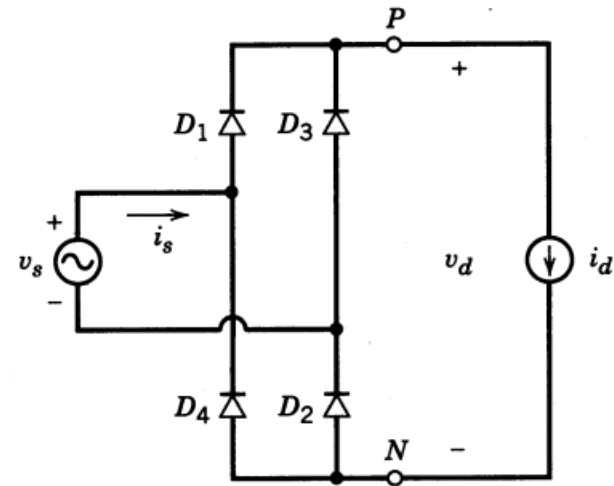
- Models case when $L/R \gg 1/120 \text{ Hz}$
- v_d waveform is the same as for a resistive load
- Power factor < 1



$$P_{avg} = V_{d,avg} I_{d,avg}$$

$$V_{d,avg} = \frac{1}{\pi} \int_0^{\pi} V_{pk} \sin(\omega t) d(\omega t) = \frac{2V_{pk}}{\pi}$$
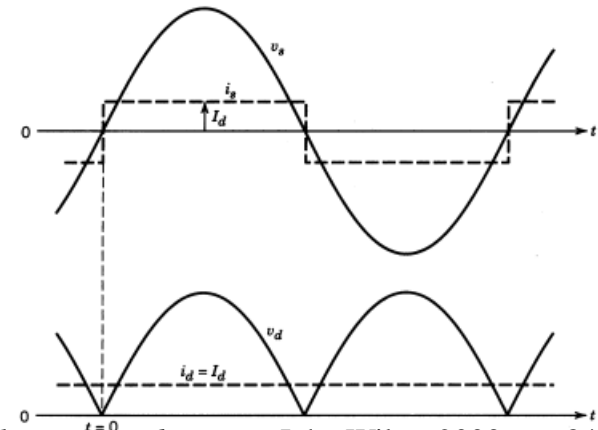
$$PF = \frac{P_{avg}}{V_{RMS} I_{RMS}} = \frac{\left(\frac{2V_{pk}}{\pi}\right) (I_{d,avg})}{\left(\frac{V_{pk}}{\sqrt{2}}\right) (I_{d,avg})} = \frac{2\sqrt{2}}{\pi} \approx 0.9$$



Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 84-85

Diode-Rectifier Bridge Input Current

- Idealized case with a purely dc output current
- Harmonic distortion in line current results in $PF < 1$

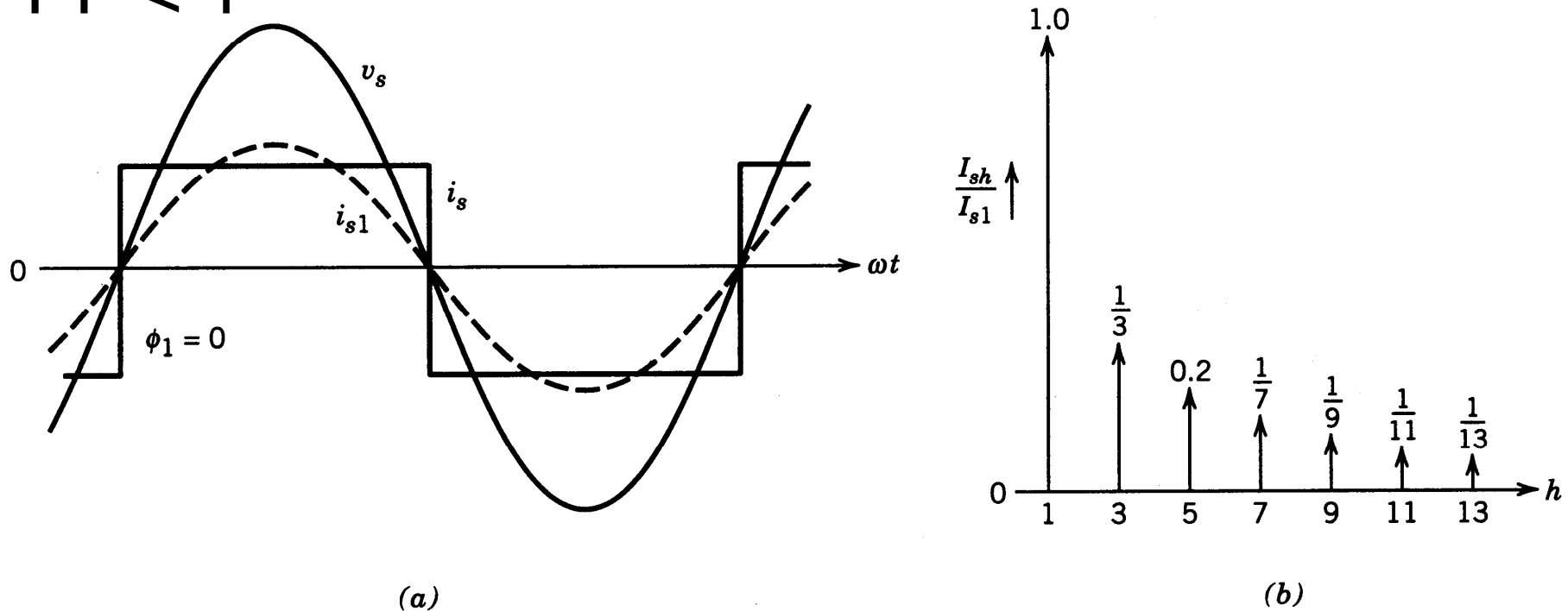


Figure 5-9 Line current i_s in the idealized case.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 86

Diode-Rectifier Bridge Analysis with AC-Side Inductance

- Output current is assumed to be purely DC; this models large inductive load
- Effect of line inductance: commutation and “softening” of line current


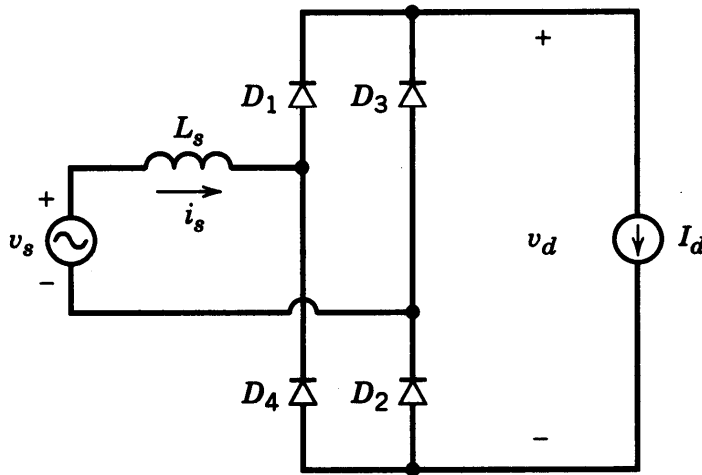


Figure 5-10 Single-phase rectifier with L_s .


Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 87

Diode-Rectifier Bridge Analysis with AC-Side Inductance --- PSPICE Analysis


- Scenario: 400 meters of #8 AWG

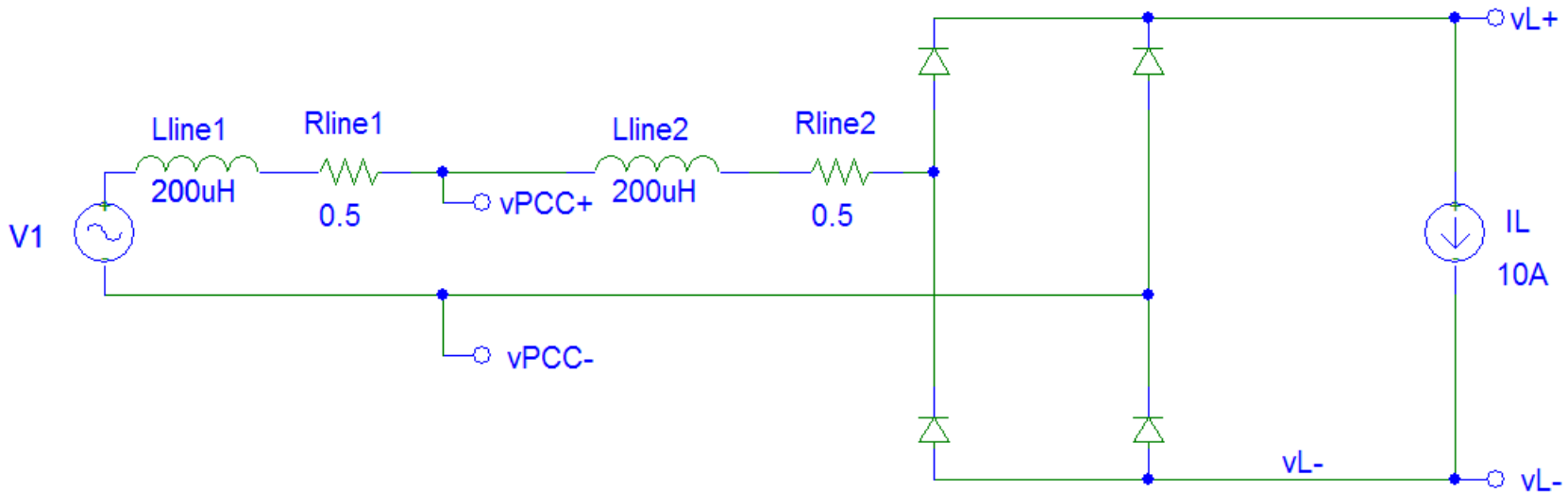

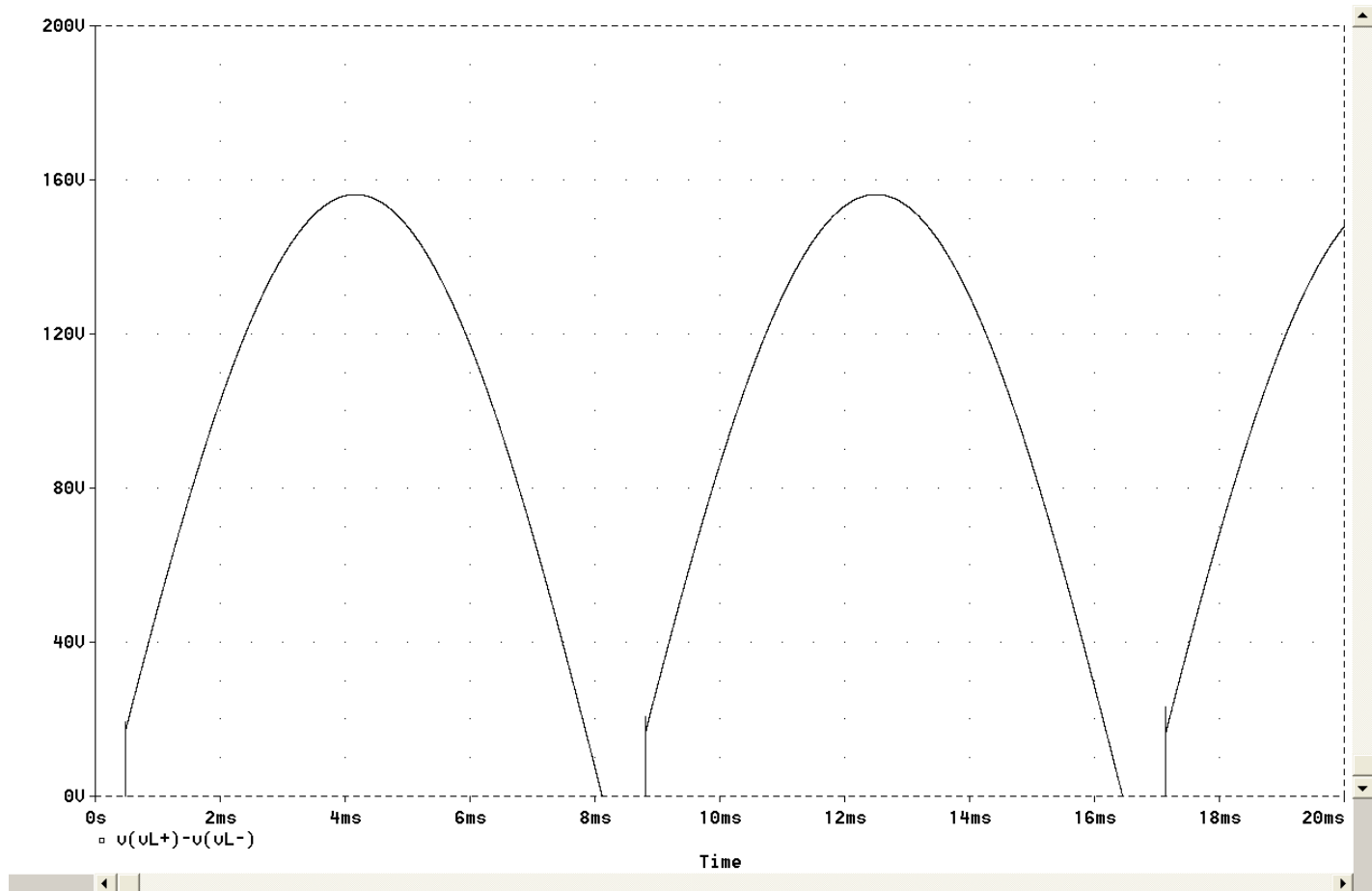
Diode-Rectifier Bridge Analysis with AC-Side Inductance --- Output Voltage



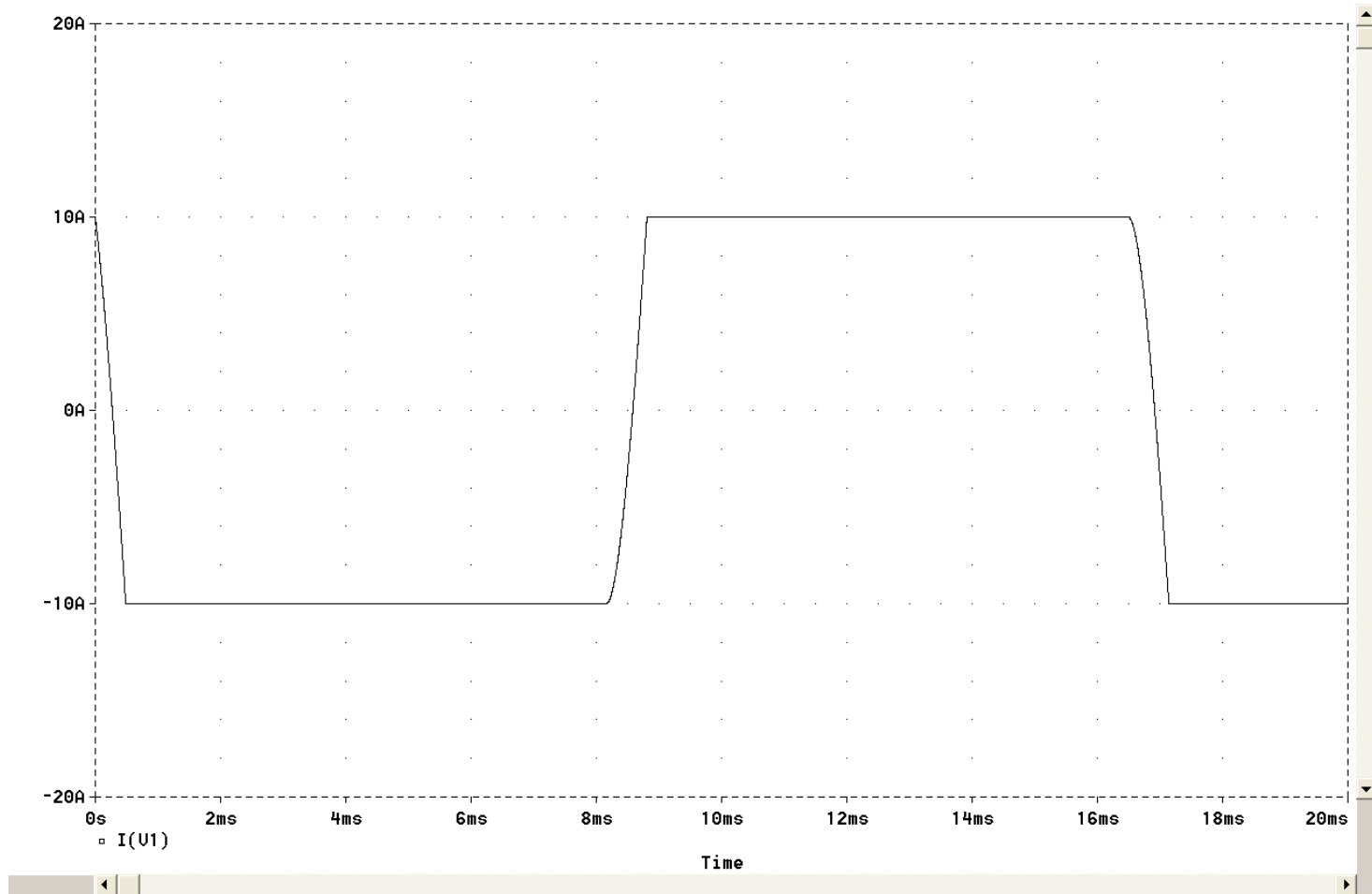
Diode-Rectifier Bridge Analysis with AC-Side Inductance --- Line Current



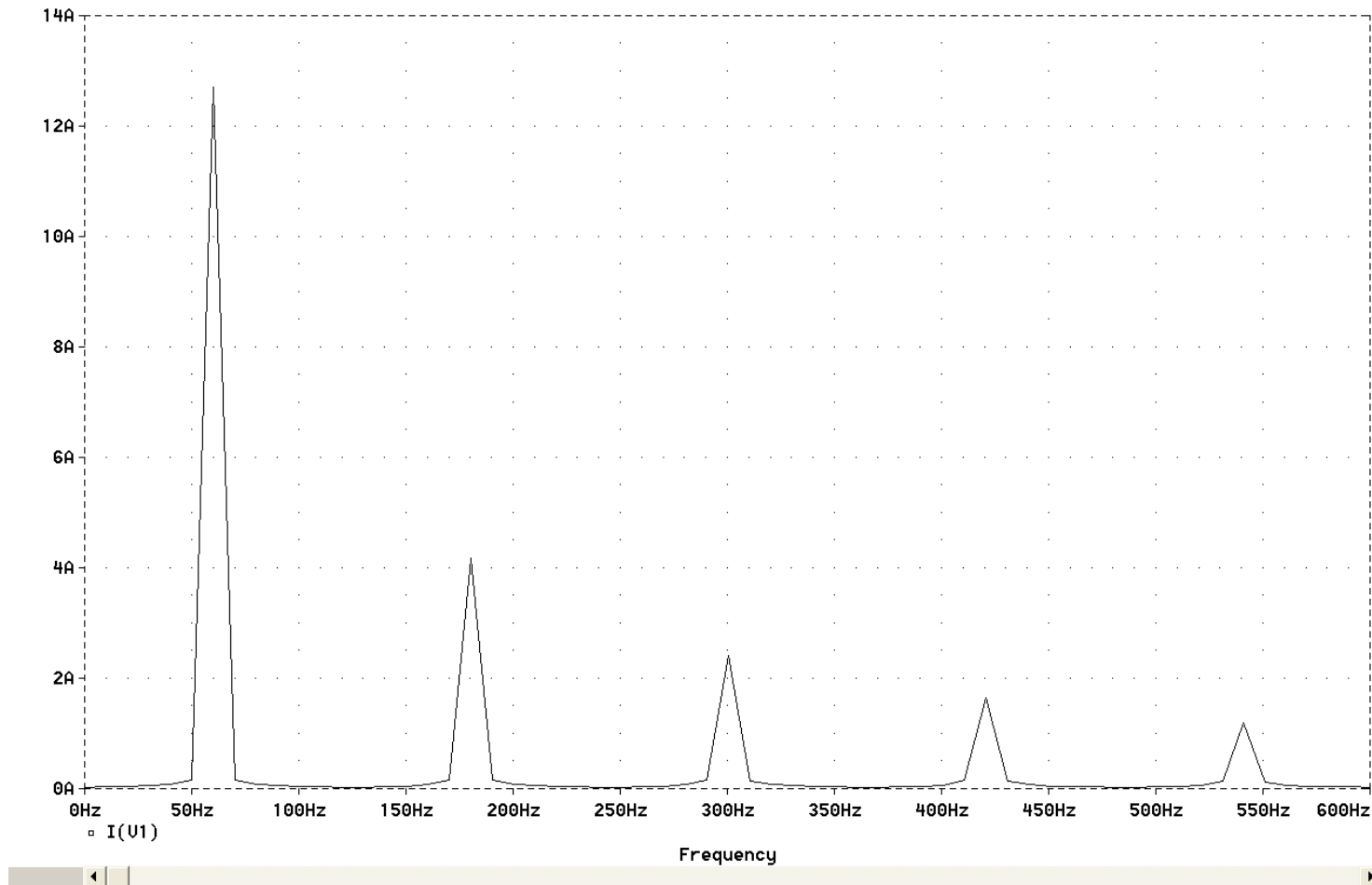
Diode-Rectifier Bridge with AC-Side Inductance --- Spectrum of Line Current



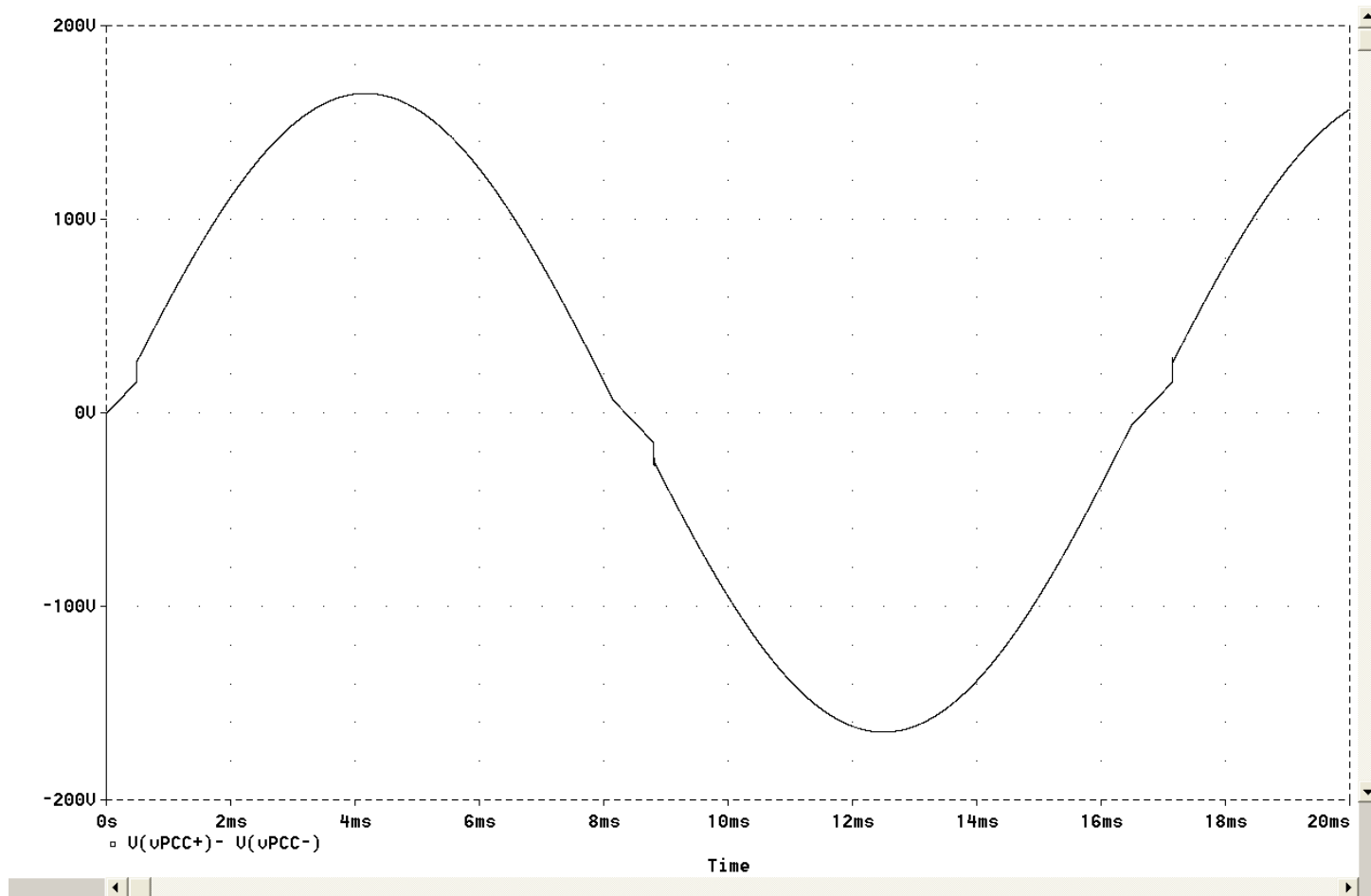Diode-Rectifier Bridge with AC-Side Inductance --- Voltage at PCC




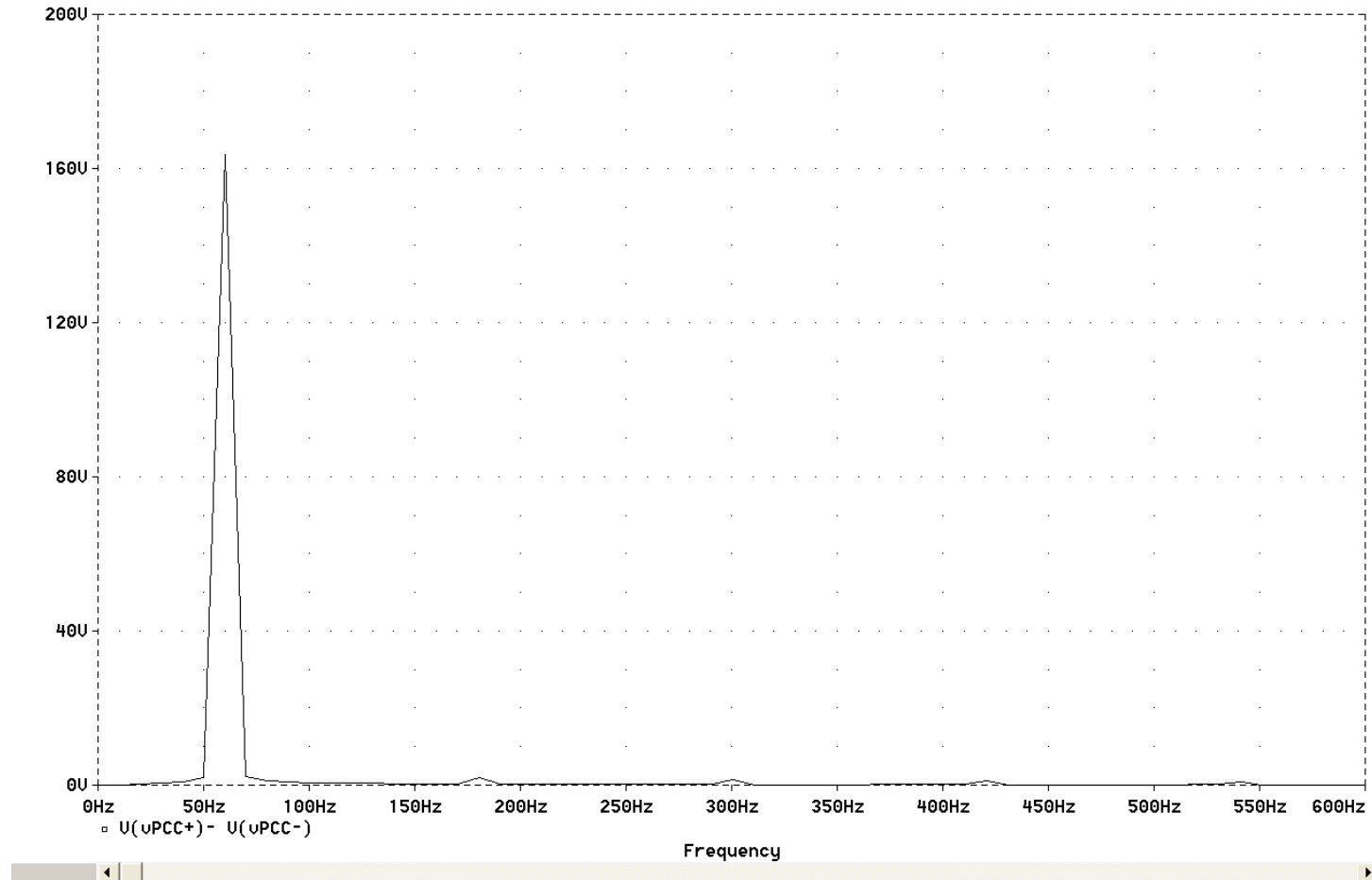Diode-Rectifier Bridge with AC-Side Inductance --- Spectrum of Voltage at PCC




Understanding Current “Commutation”

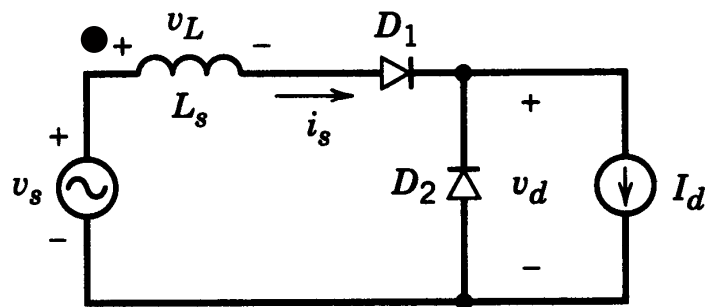- Commutation is process by which flowing current switches from one diode to the other
- With $L_s=0$, D1 and D2 snap ON and OFF infinitely fast
 - D1 is ON and D2 is OFF for positive half-cycle of line



(a)

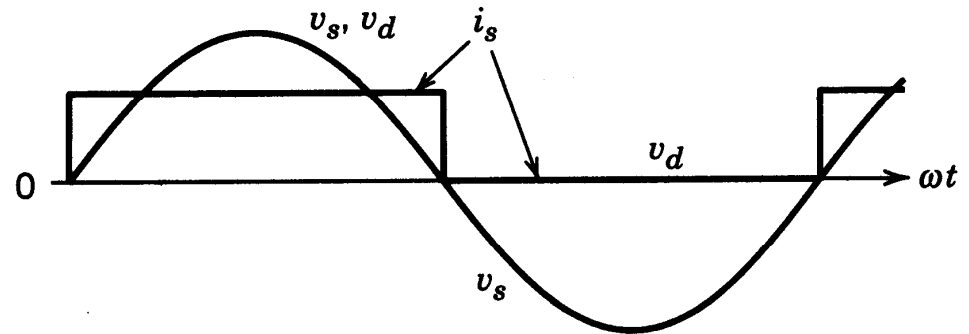

(b)

Figure 5-11 Basic circuit to illustrate current commutation. Waveforms assume $L_s = 0$.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 87

Current Commutation (cont.)

- Things are not as simple if line inductance is included
 - (All lines have some inductance)
- During “commutation” interval, both diodes are on

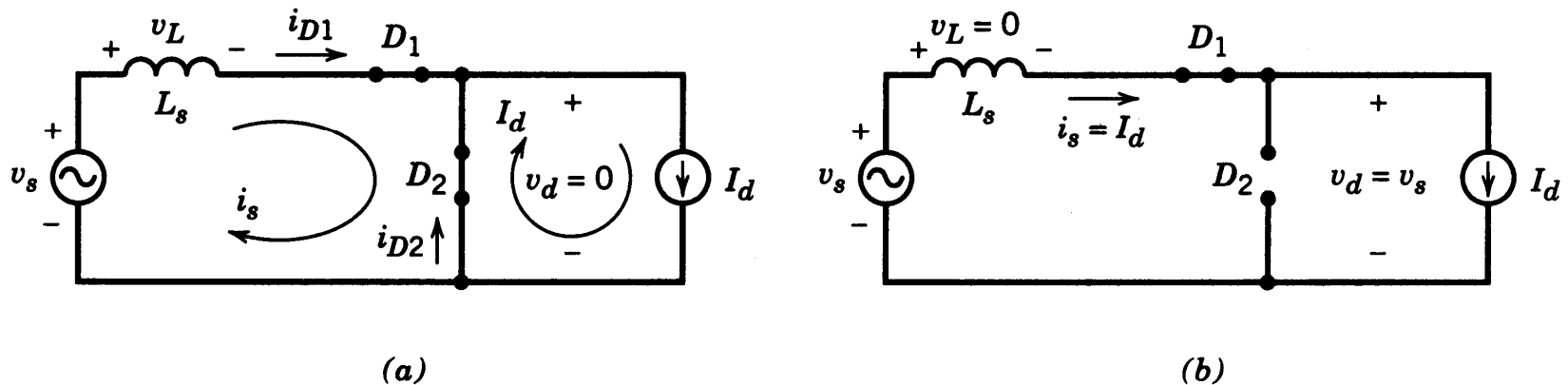


Figure 5-12 (a) Circuit during the commutation. (b) Circuit after the current commutation is completed.

Current Commutation (cont.)

- Shows the volt-seconds needed to commutate current
- $0 < t < u$ is the “commutation interval” when both diodes are ON

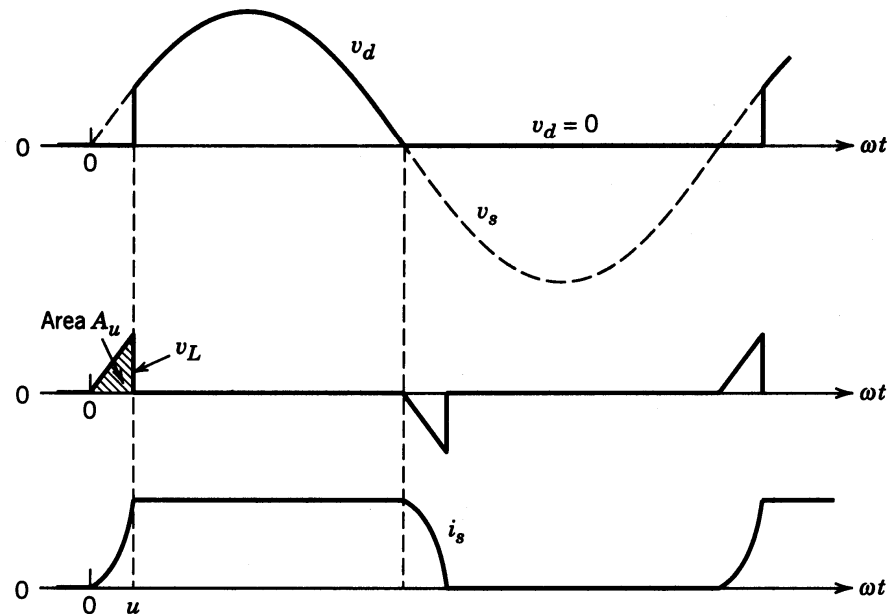



Figure 5-13 Waveforms in the basic circuit of Fig. 5-11. Note that a large value of L_s is used to clearly show the commutation interval.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp.88

“Load Regulation”

- Inductance causes output voltage to be lower than that for basic half-wave rectifier
- Average output voltage decreases with output load current
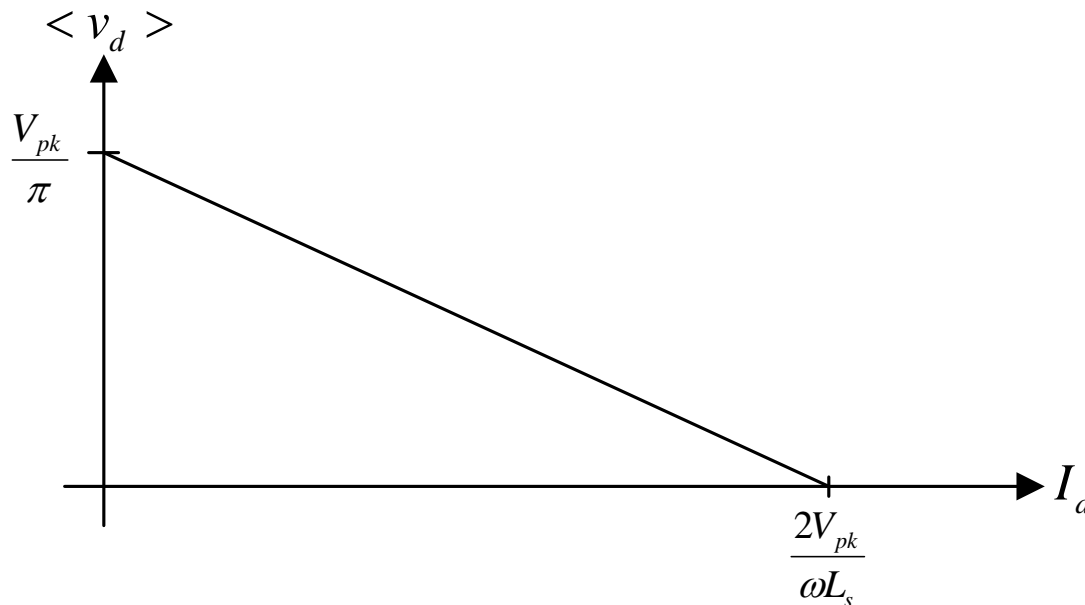
$$\langle v_d \rangle = \frac{V_{pk}}{2\pi} \int_u^{\pi} \sin x dx = \frac{V_{pk}}{2\pi} (1 + \cos u) = \frac{V_{pk}}{\pi} \left(1 - \frac{\omega L_s I_d}{2V_{pk}} \right)$$



Current Commutation in Full-Bridge Rectifier

Commutation process:

$\omega t < 0$: D3 and D4 are ON

$\omega t = 0^+$: v_s becomes positive and D1 and D2 turn ON; $v_d = 0$

since all 4 diodes are ON

$\omega t = u$: current in D3 and D4 has dropped to zero and they turn OFF; output voltage snaps up to input line voltage

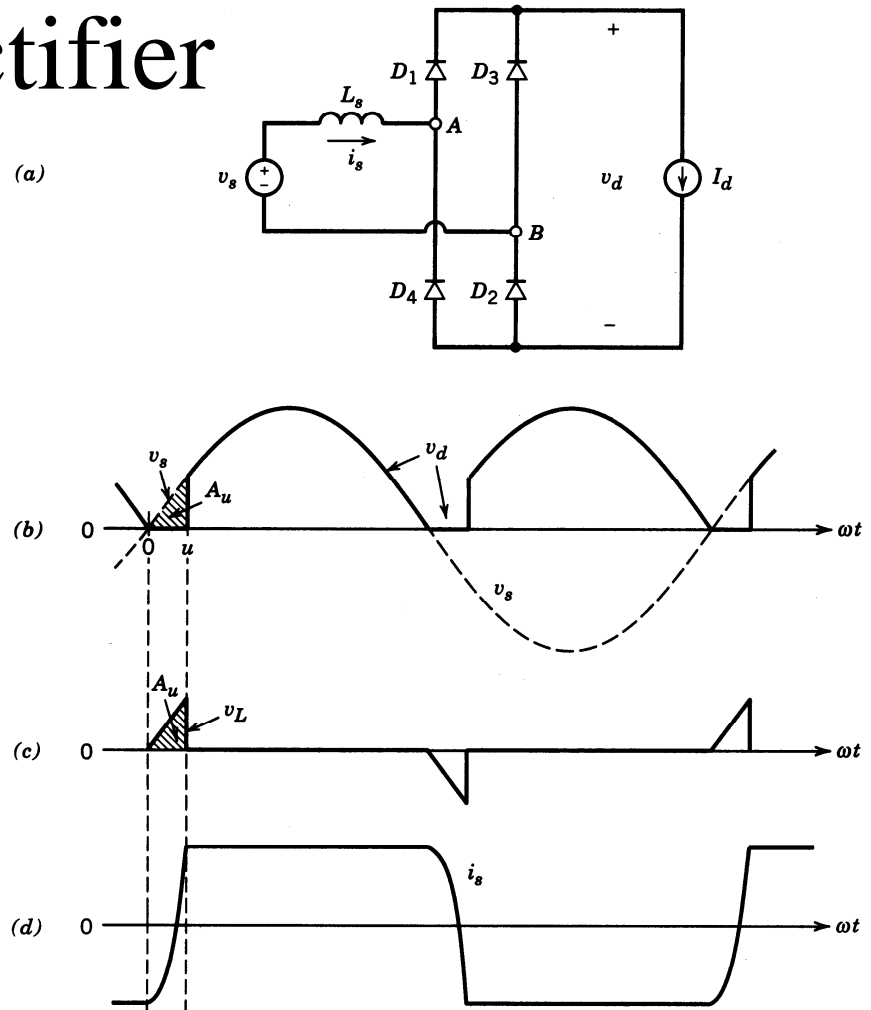


Figure 5-14 (a) Single-phase diode rectifier with L_s . (b) Waveforms.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 90

Three-Phase, Full-Bridge Rectifier

- Commonly used in high power applications


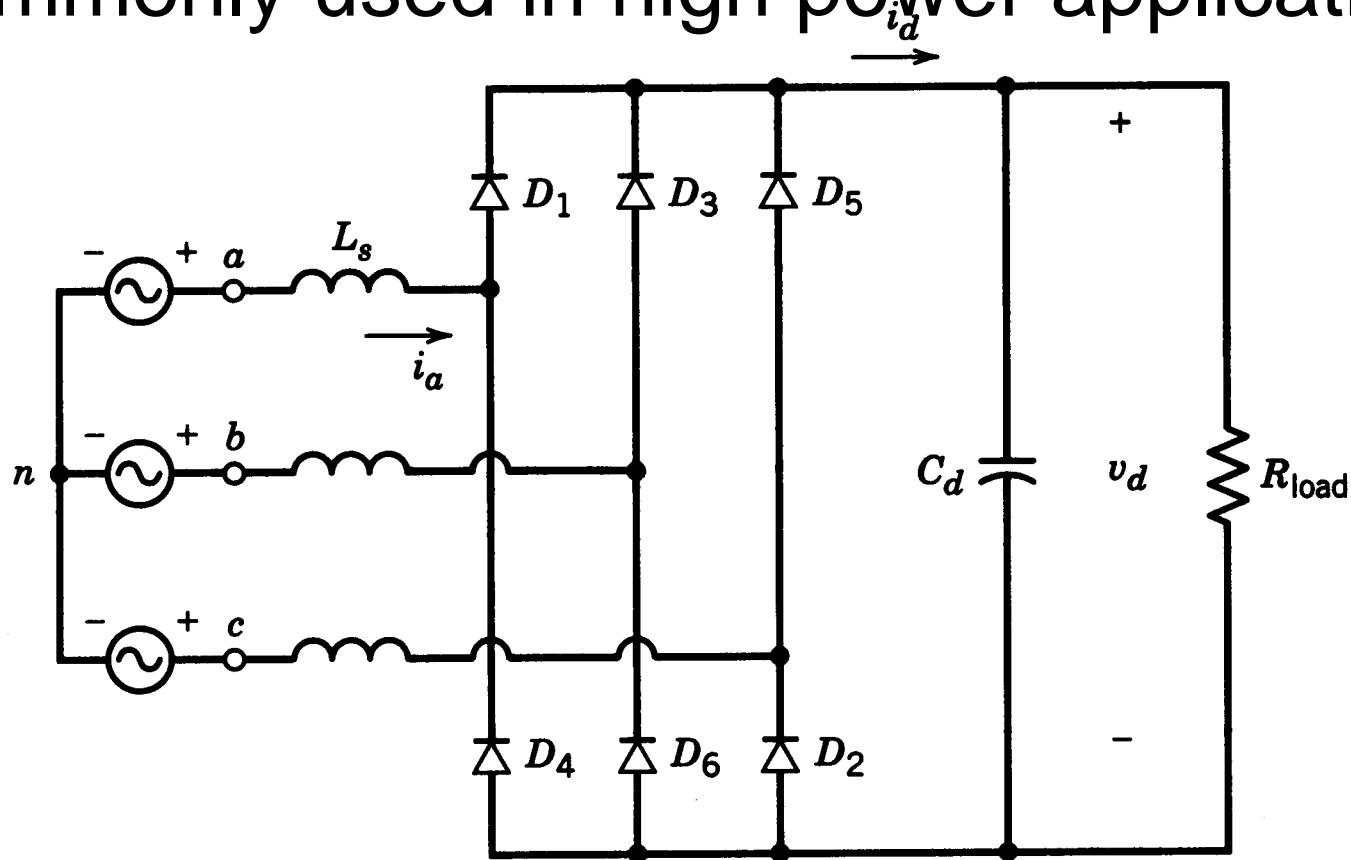


Figure 5-30 Three-phase, full-bridge rectifier.


Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 103

Three-Phase Rectifier with Current Source Load

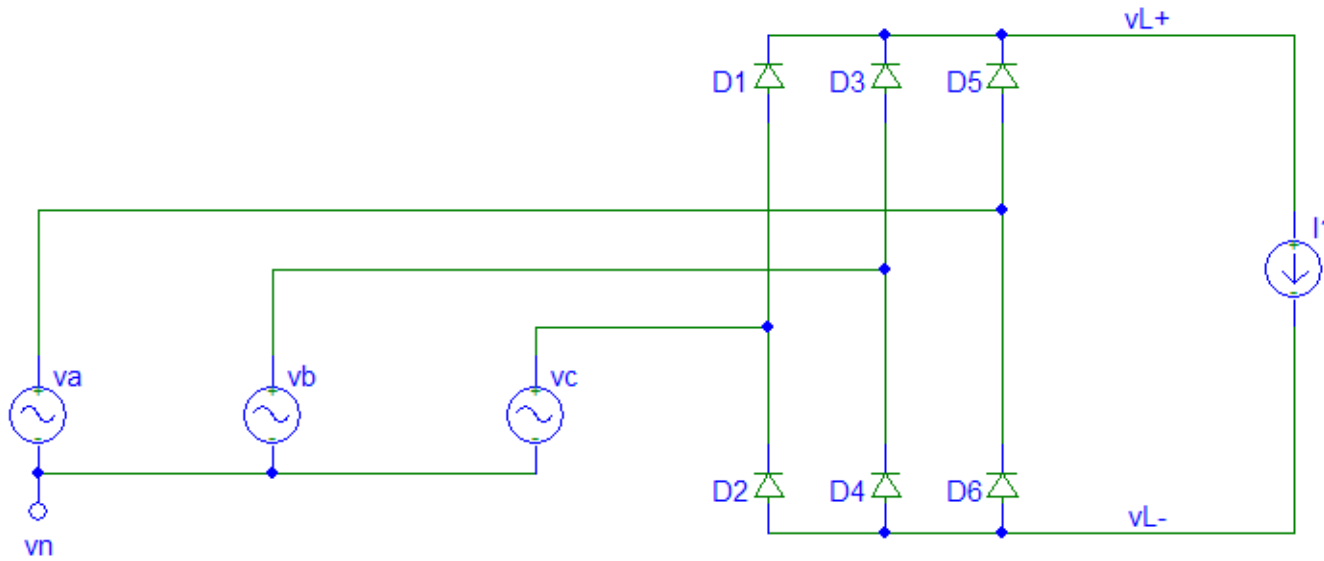- Simplified with line inductance = 0 and current source load
- Neutral current = 0
- Phase currents do have harmonics



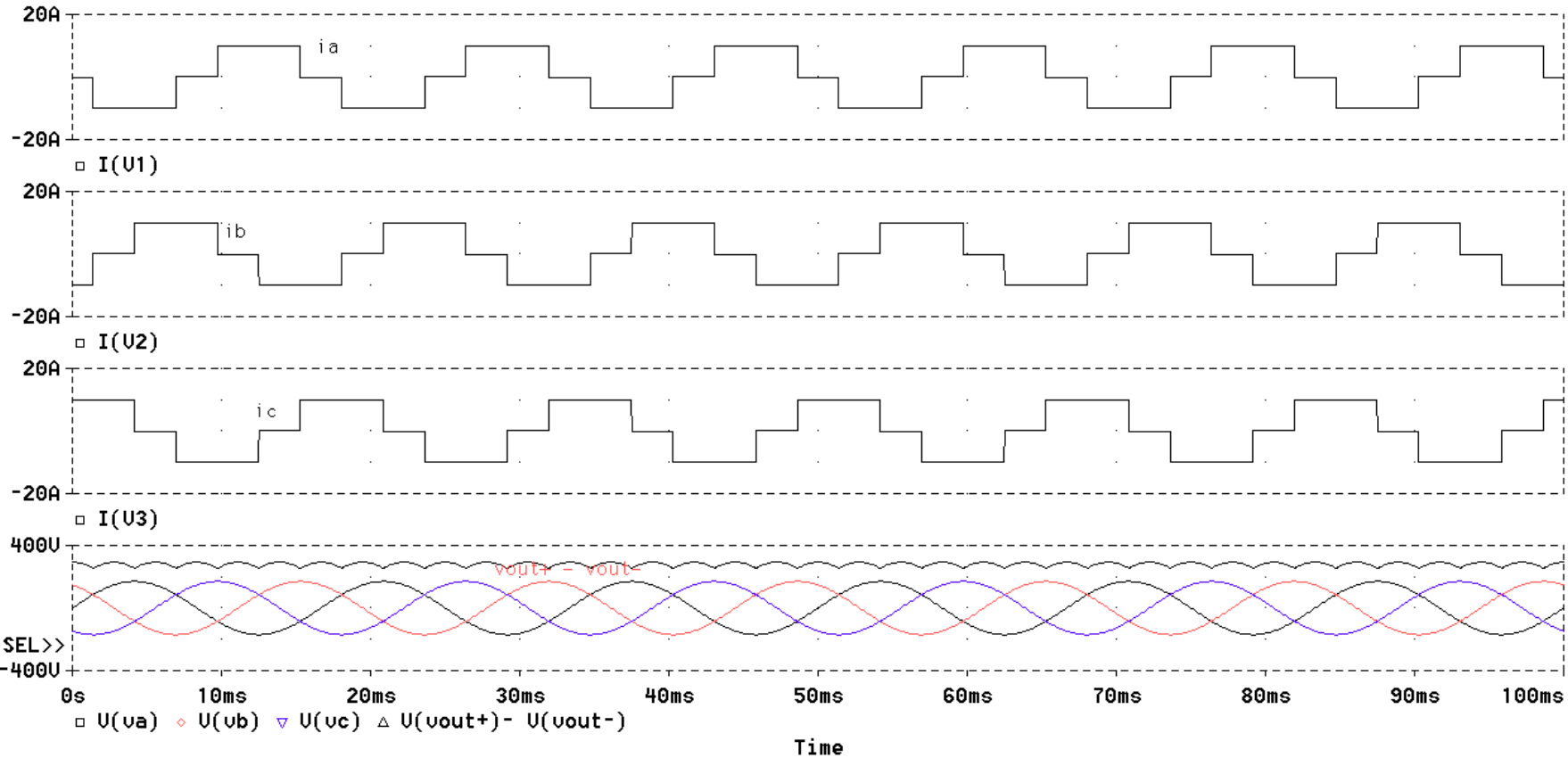Three-Phase Rectifier with Current Source Load



Three-Phase, Full-Bridge Rectifier

- Shown for output DC current source load

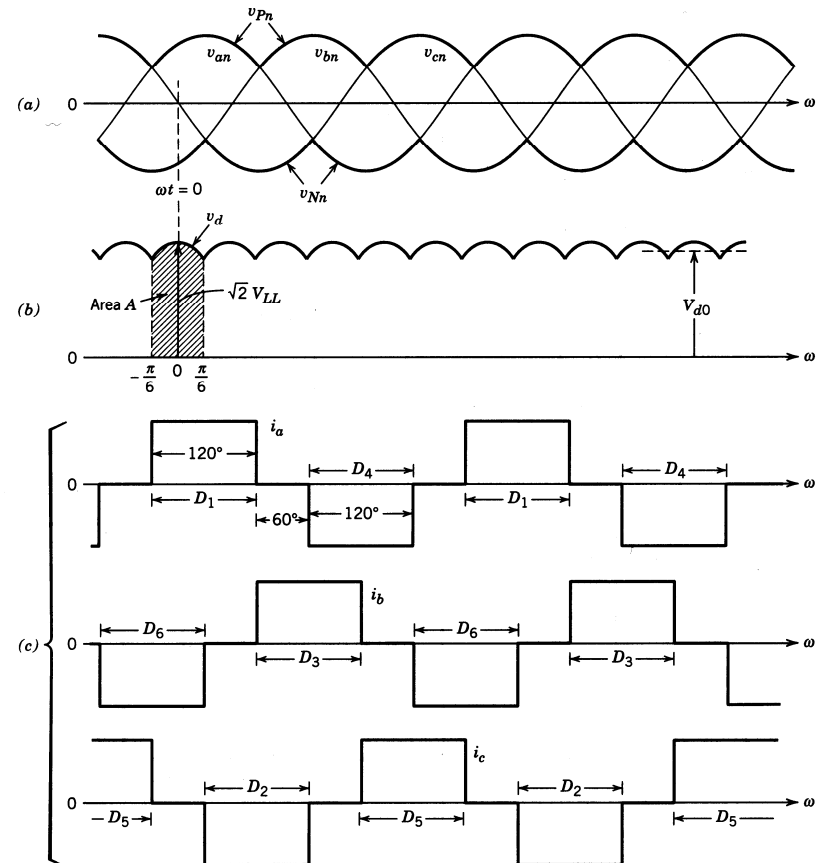


Figure 5-32 Waveforms in the circuit of Fig. 5-31.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 104

Three-Phase, Full-Bridge Rectifier: Line Current

- Assuming output current to be purely dc and zero ac-side inductance
- No “triplens”, i.e. 3rd, 9th, etc. harmonics


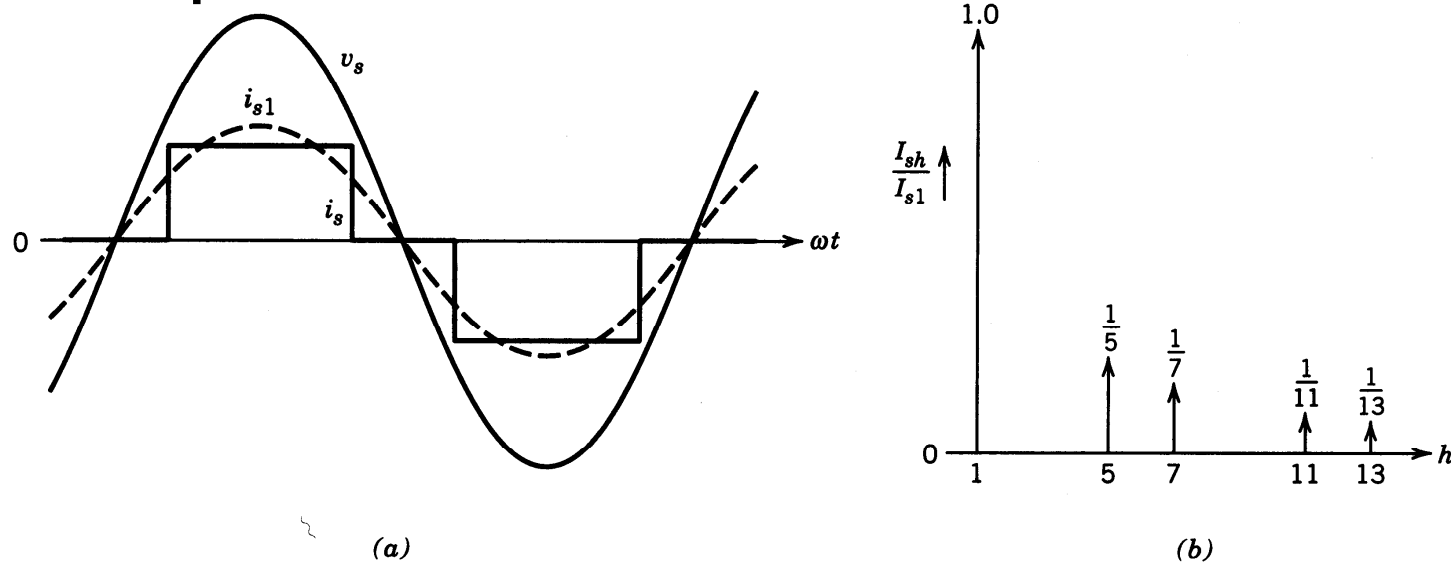


Figure 5-33 Line current in a three-phase rectifier in the idealized case with $L_s = 0$ and a constant dc current.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 106


Three-Phase Rectifier with Resistive Load

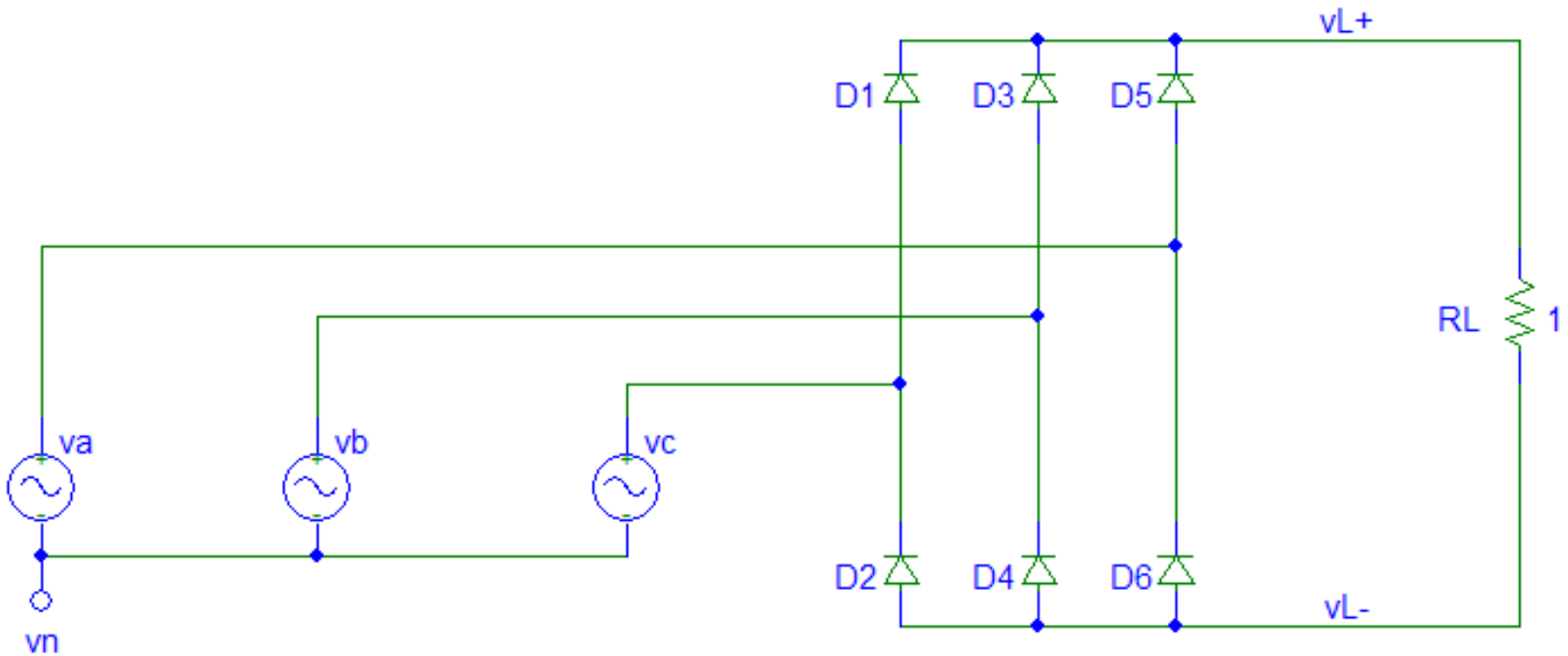- Resistive load models high power factor load




3-Phase Rectifier with Resistive Load --- Output

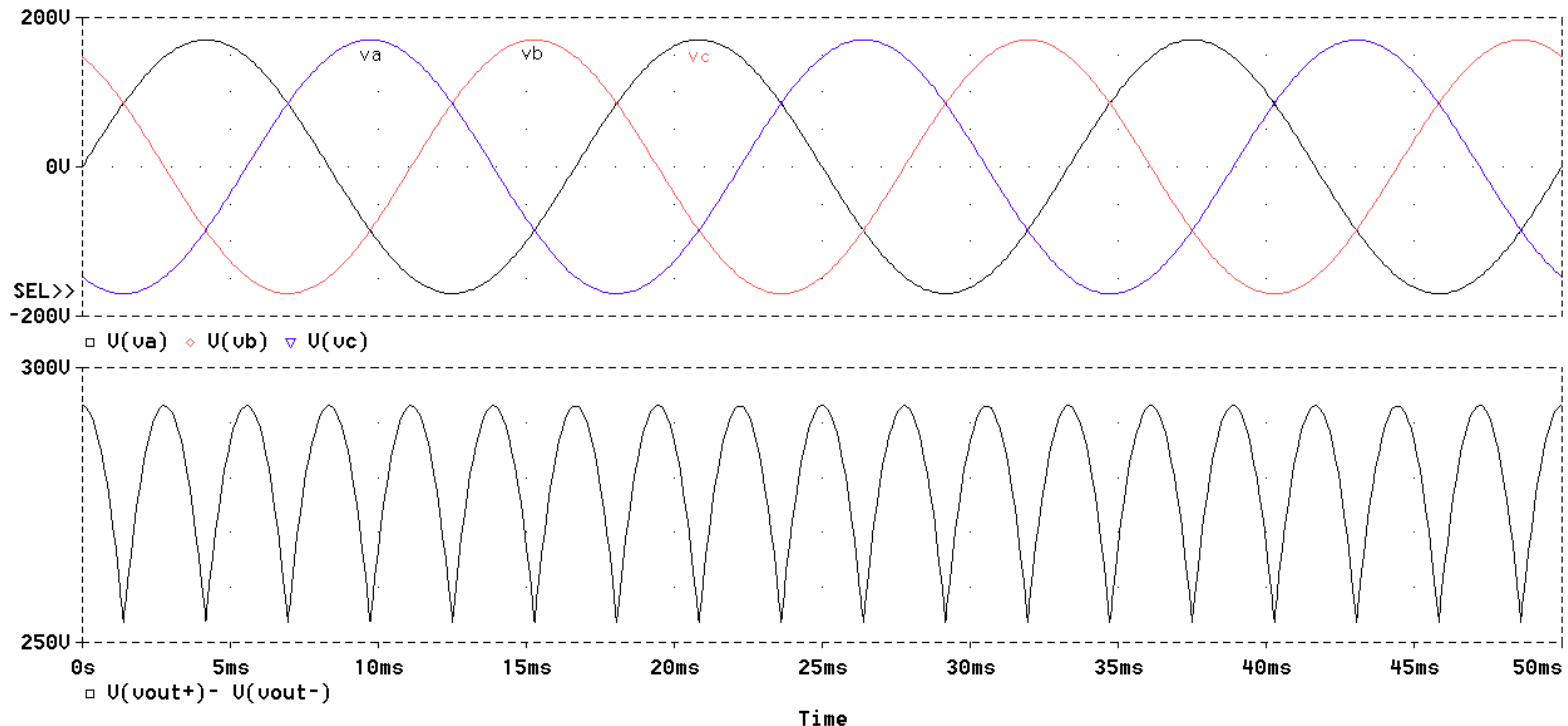- Fundamental of ripple frequency = 360 Hz
- Peak value is $\sqrt{3}$ x peak of line = 294V




Three-Phase Rectifier with Resistive Load and Capacitor Filter

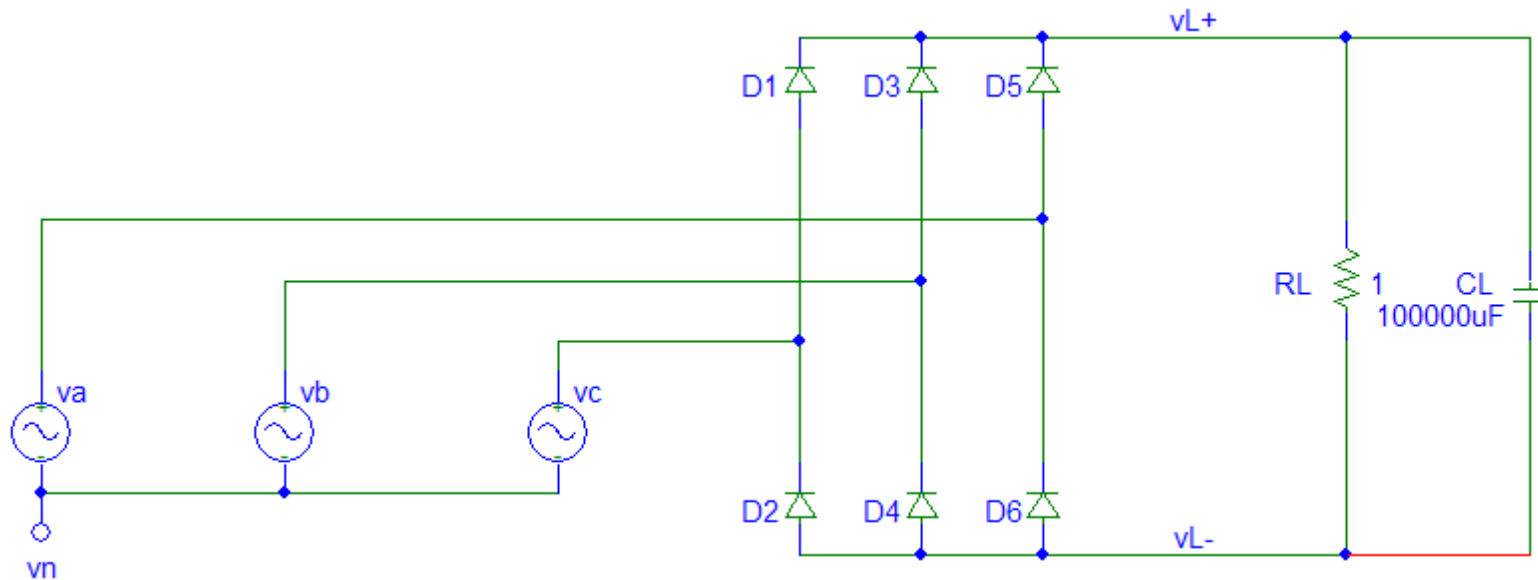
- Note that a smaller capacitor can be used for the 3 phase rectifier compared to single phase rectifier, because (1) Ripple is smaller and (2) Ripple frequency is higher



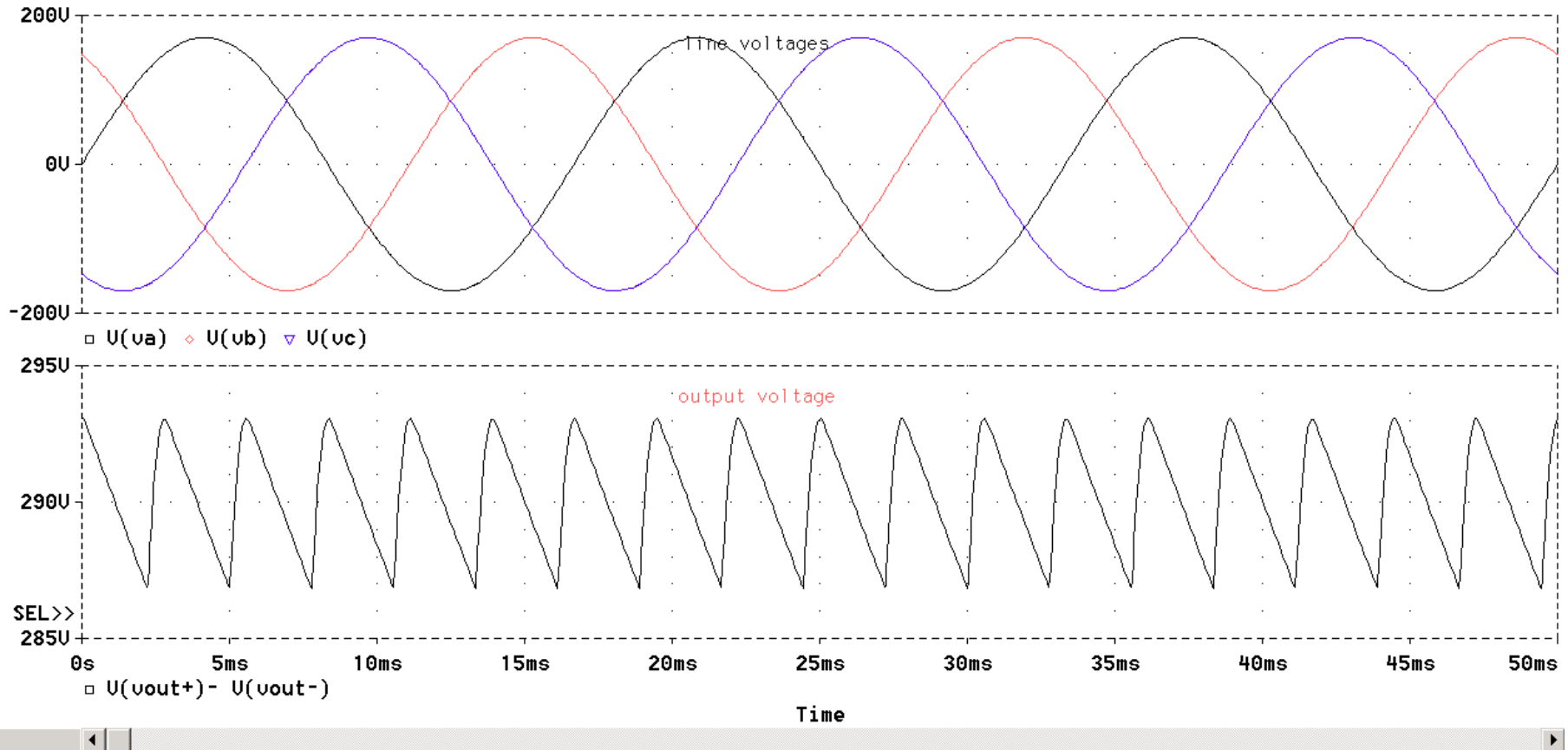Three-Phase Rectifier with Resistive Load and Capacitor Filter




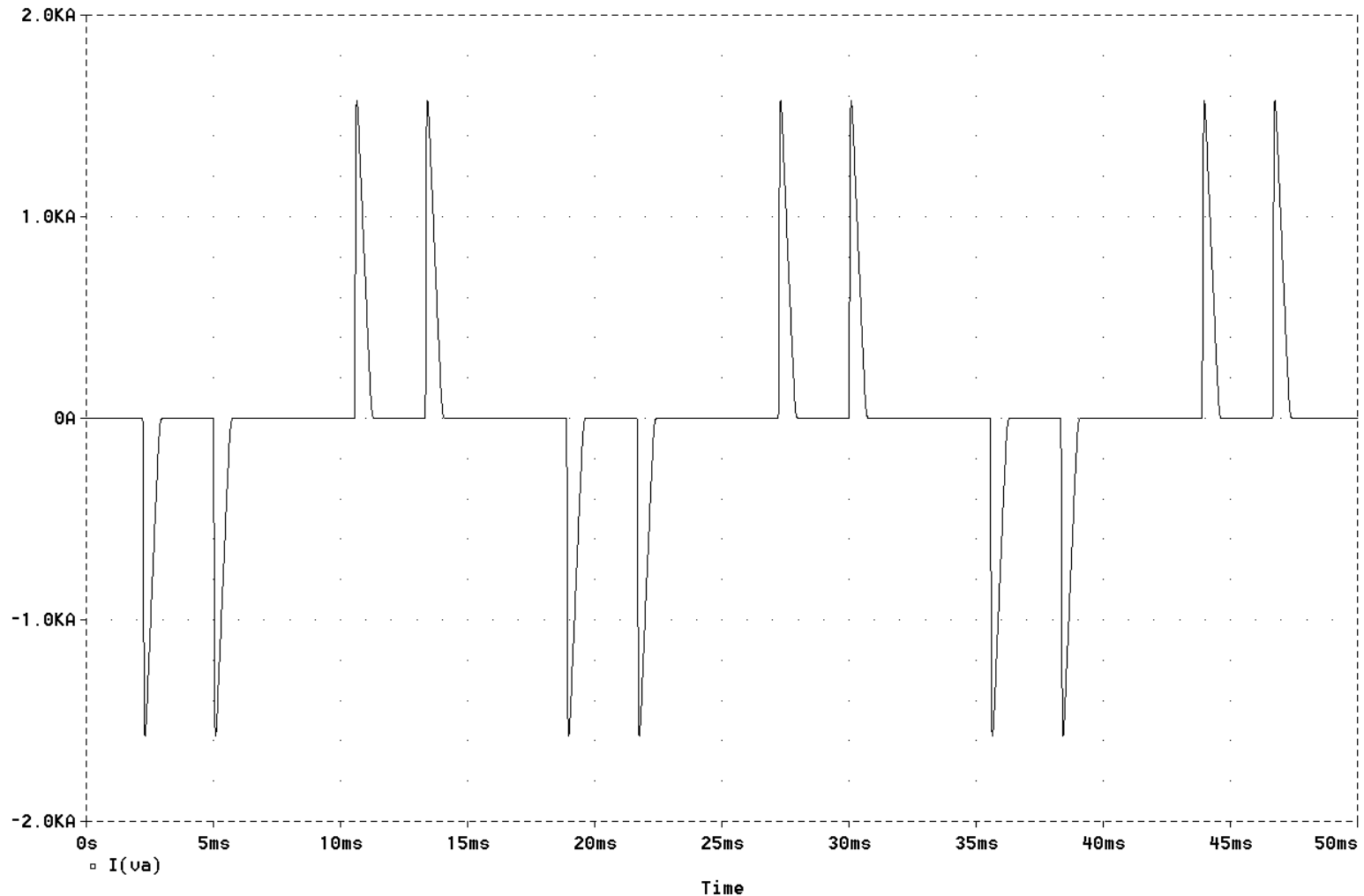Three-Phase Rectifier with Resistive Load and Capacitor Filter --- Phase Current



3-Phase Rectifier with Resistive Load and Capacitor Filter --- Phase Current Spectrum

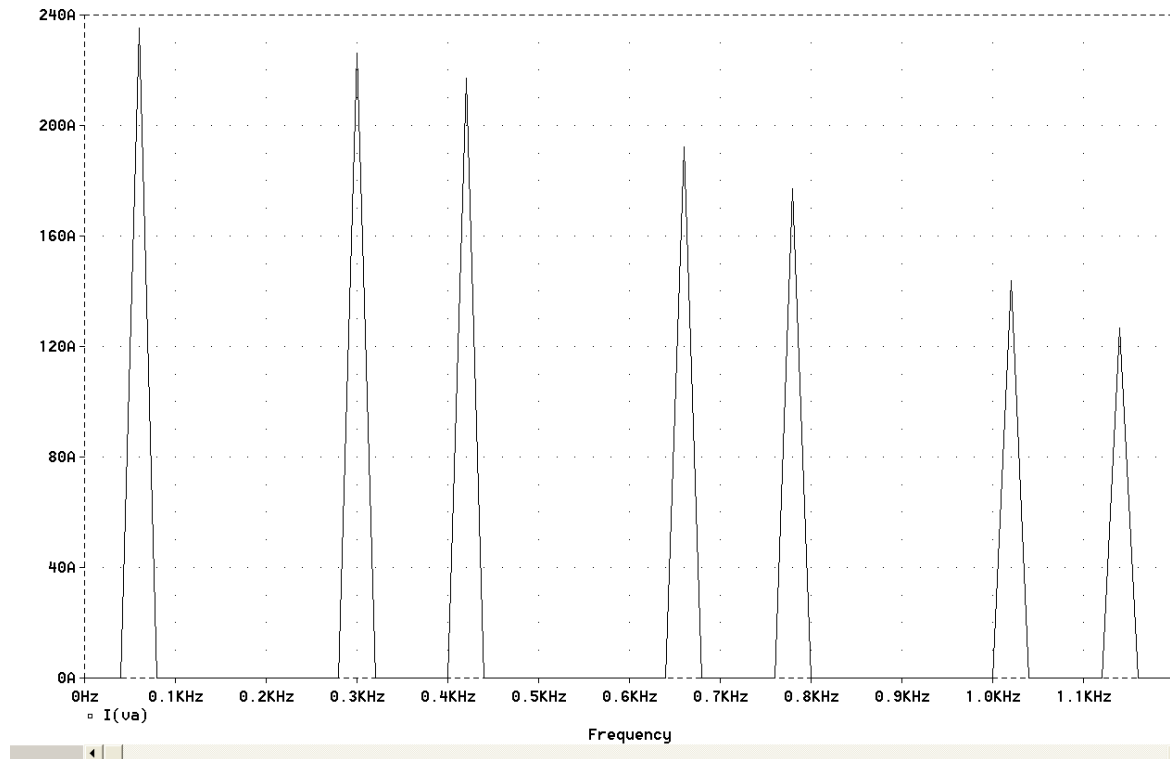- Phase current contains 1st, 5th, 7th, 11th, 15th ... harmonics



Mitigating Strategies

- Harmonic trap
 - Filter designed to pass fundamental and attenuate harmonics
- 12-pulse rectifier: harmonics are 11th, 13th, 23rd, 25th, ...
 - 12-pulse eliminates 5th, 7th, 17th, 19th, ... harmonics
 - Requires Y-Y and Delta-Y transformers, and 12 diodes

Three-Phase, Full-Bridge Rectifier: Redrawn

- Two groups with three diodes each

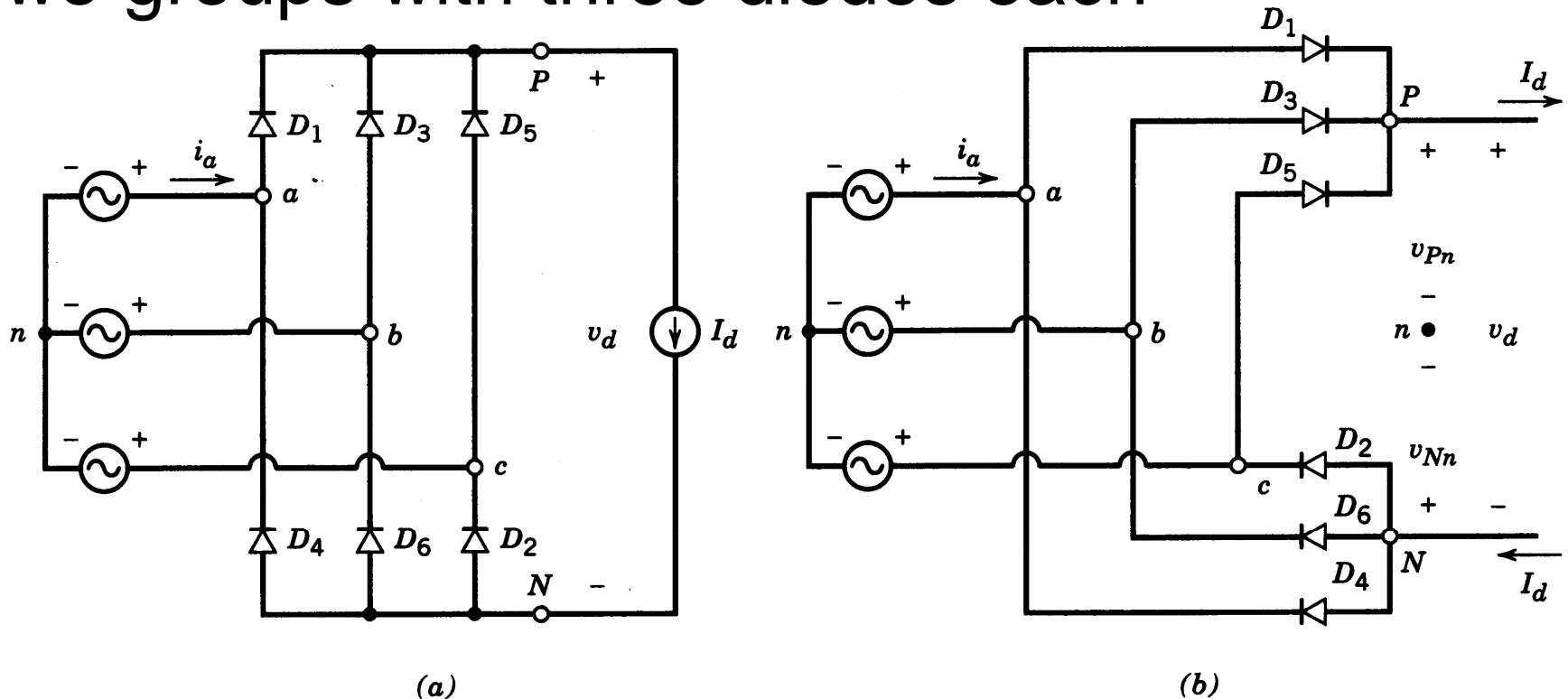


Figure 5-31 Three-phase rectifier with a constant dc current.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 103

Three-Phase, Full-Bridge Rectifier

- Including the ac-side inductance means that we have another commutation process

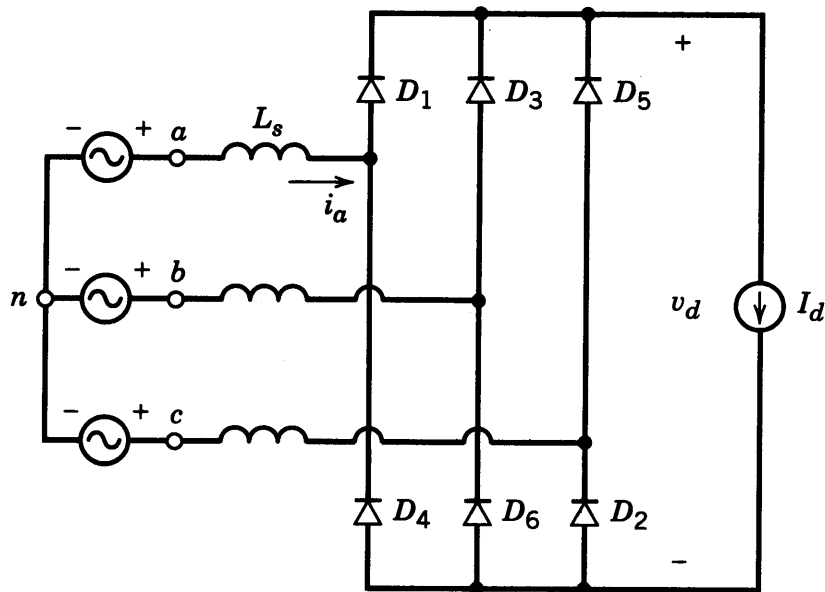


Figure 5-34 Three-phase rectifier with a finite L_s and a constant dc current.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 106

3-Phase Rectifier: Current Commutation

- Output current is assumed to be purely dc

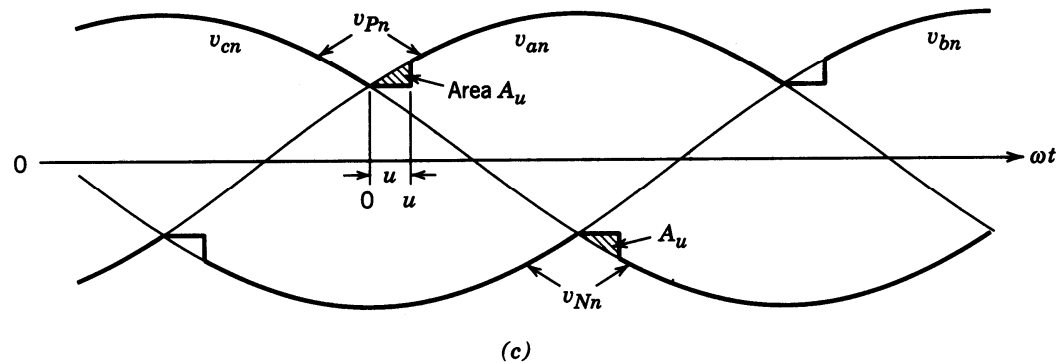
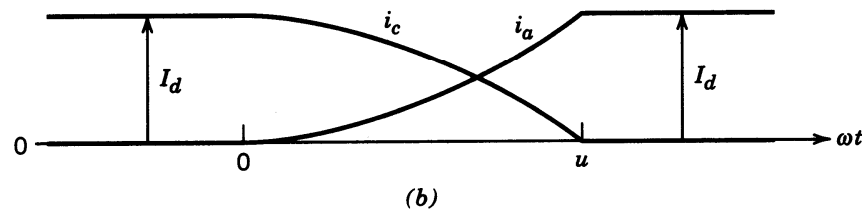
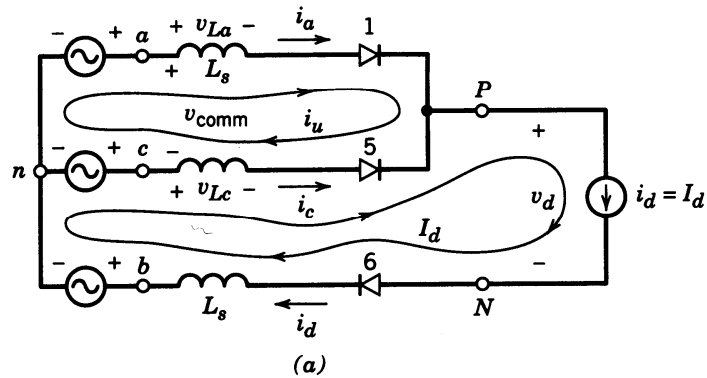


Figure 5-35 Current commutation process.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 107

Ramifications of Harmonics

- Triplens can cause buildup of neutral current; neutral current can exceed phase current
- Noise in power lines
- Buzzing of power panels

A Three-Phase, Four-Wire System

- With single-phase nonlinear loads, there can be a neutral current

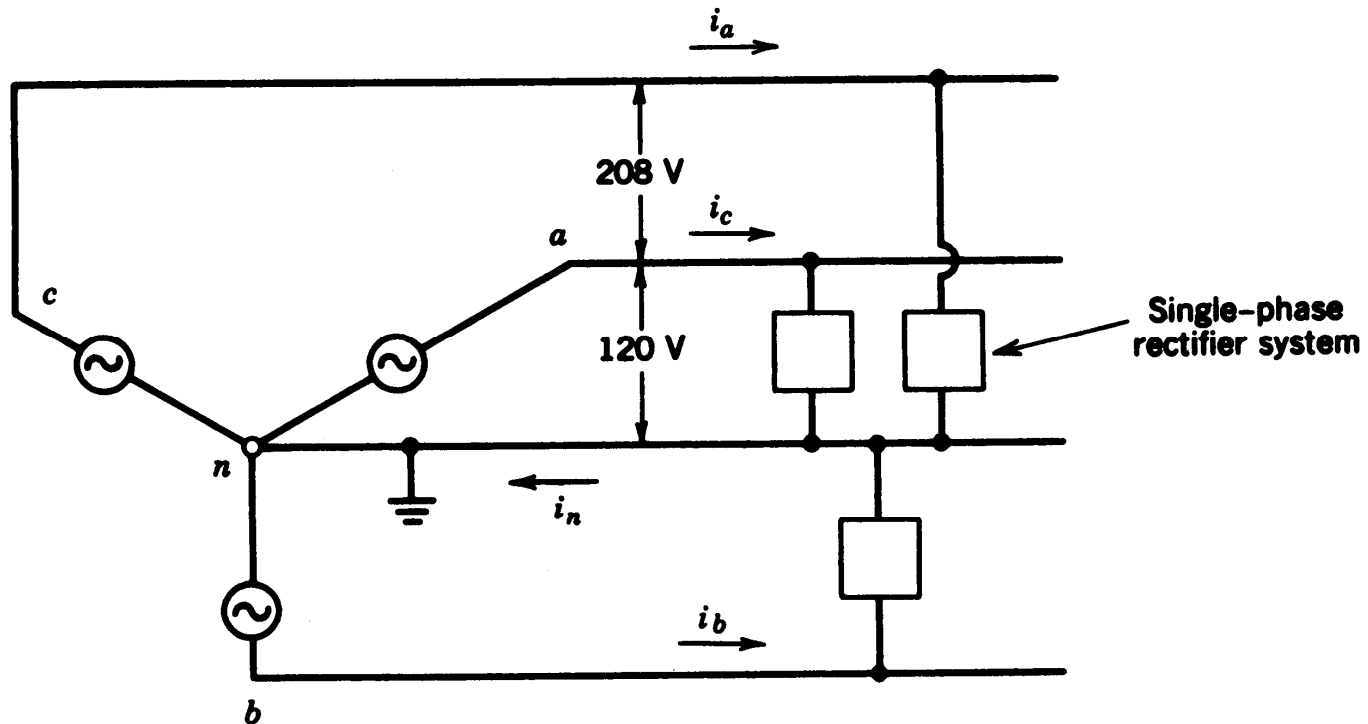


Figure 5-28 Three-phase, four-wire system.

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 101

Current in a 3-Phase, Four-Wire System

- The neutral current can be very high if driving nonlinear loads line to neutral
- If line currents are highly discontinuous, the neutral current can be as large as 1.73xline current 3rd harmonic
- Note 3rd harmonic here


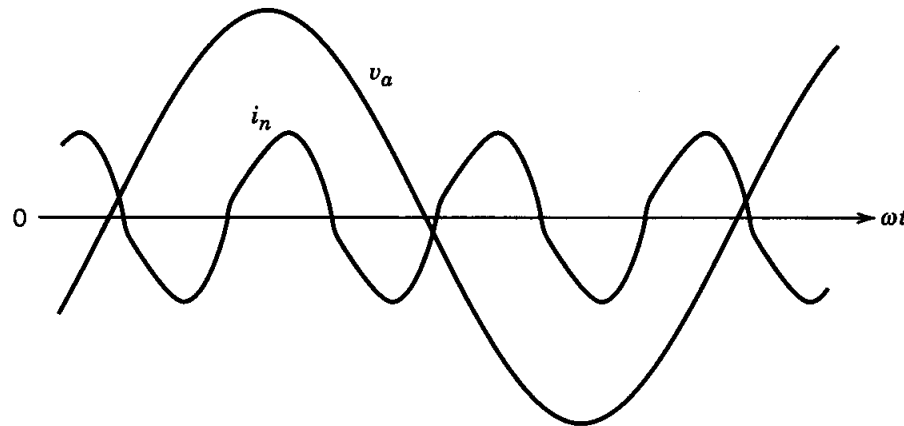



Figure 5-29 Neutral-wire current i_n .

Reference: Mohan, Undeland and Robbins, *Power Electronics, Converters, Applications and Design*, John Wiley, 2003, pp. 102

Simulation of Simple Case

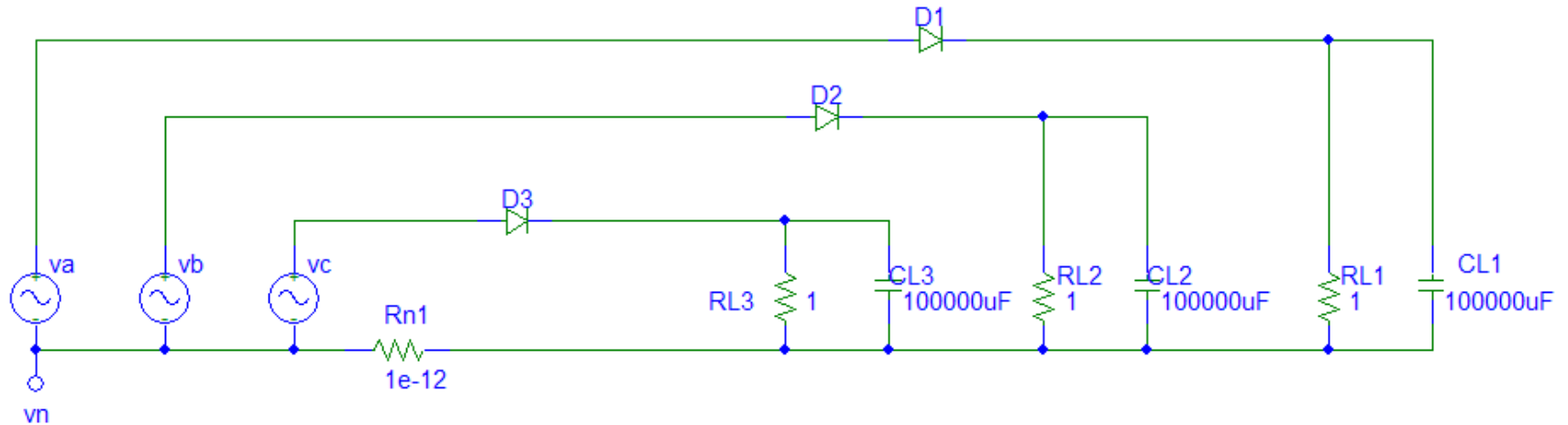

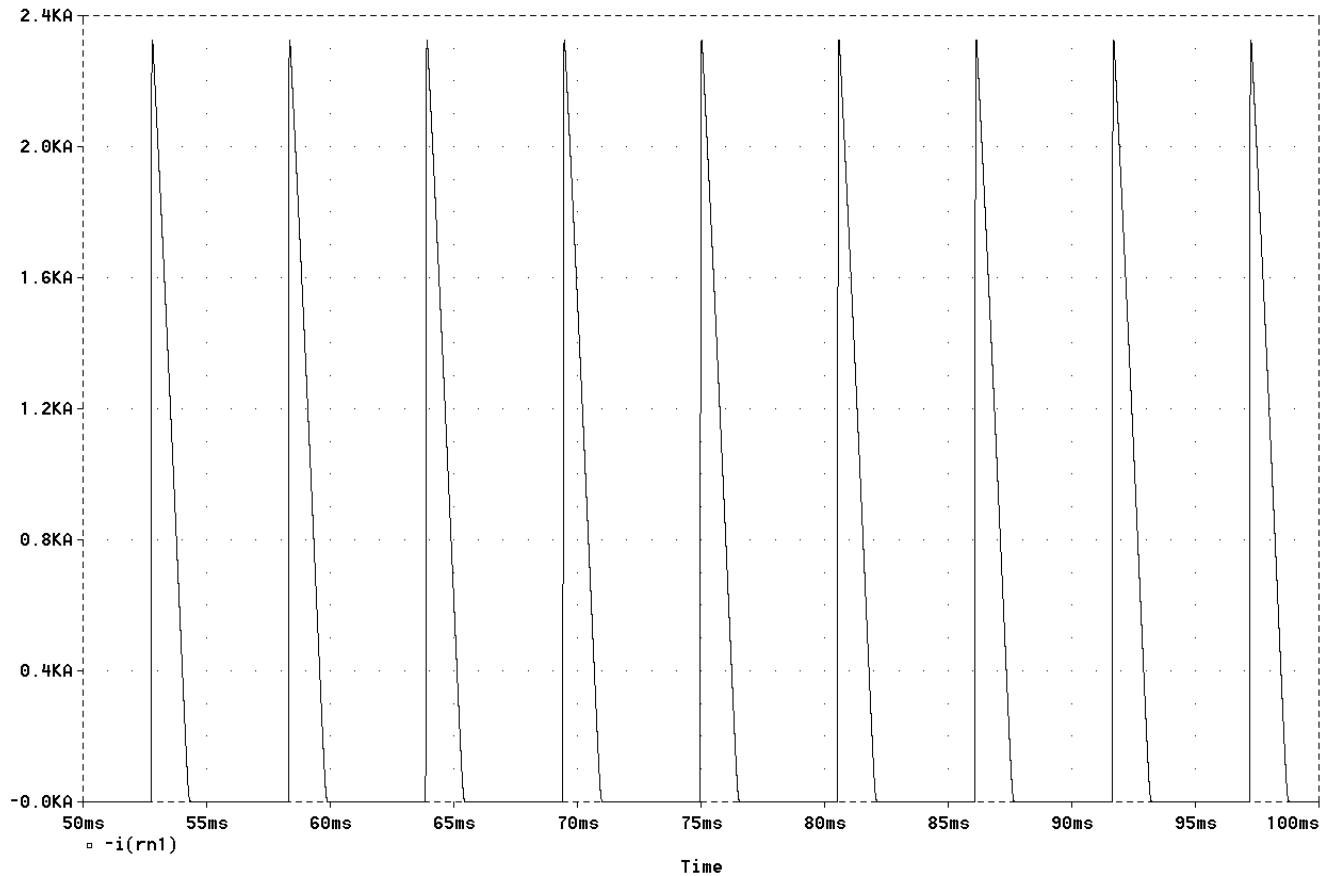Simulation of Simple Case --- Neutral Current



Simulation of Simple Case --- Spectrum of Neutral Current

