



# Power Quality

## Notes 2-2 (AK)

Marc Thompson, Ph.D.  
Senior Managing Engineer  
Exponent  
21 Strathmore Road  
Natick, MA 01760

Alex Kusko, Sc.D, P.E.  
Vice President  
Exponent  
21 Strathmore Road  
Natick, MA 01760

Adjunct Associate Professor of Electrical  
Engineering  
Worcester Polytechnic Institute  
Worcester, MA 01609

# Review

- Voltage distortion
- CBEMA curve
- Harmonics
- Calculation of harmonic voltages
- IEEE Std. 519


# Class #2 - Hour #2 (4/12/05)

## Harmonic Current Effects

- Sources of harmonic currents
- Case study, plastic extrusion plant
- Case study, GE diagnostic imaging system
- IEEE Paper, “Effects of Harmonics on Equipment”
- Resonance, capacitors

# Sources of Harmonic Currents

- Static power converter, ASD, source of harmonic current

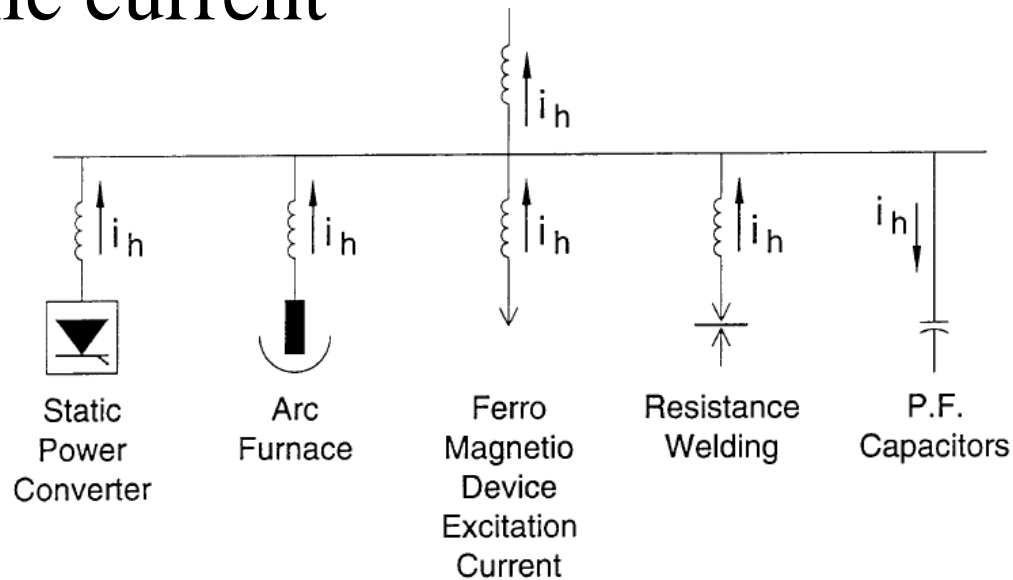

**Fig 8.1**  
**Modeling Nonlinear Loads by Current Sources**

Reference: IEEE Standard 519-1992, "IEEE Recommended Practices and Requirements for Harmonic Control in Electrical Power Systems," pp. 55

# Case Study: “Power Harmonic Problems at a Plastic Extrusion Plant”

- Original: utility transformer, 300 kVA
- Extruder, thyristor DC drive, 250 hp
- Poor power factor, 0.57

Reference: Nosh Medora and Alex Kusko, “Power Harmonic Problems at a Plastic Extrusion Plant,” *IEEE IAS Annual Conference*, October 1995

# Power Measurements

TABLE 1  
POWER MEASUREMENTS PERFORMED  
AT PLASTIC EXTRUSION PLANT

*Transformer: 300-kVA 13.8 kV to 480 V*  
*Extruder: 250-HP Thyristor DC Adjustable Speed Drive*

Measured Parameter	Phase A
Line Voltage (l-l)	468 V
Line Current ( $I_l$ )	490 A
Real Power (P)	226 kW
Reactive Power (Q)	326 kvar
Apparent Power (S)	397 kVA
Power Factor (p.f.)	0.57

Reference: Nosh Medora and Alex Kusko, "Power Harmonic Problems at a Plastic Extrusion Plant," *IEEE IAS Annual Conference*, October 1995

# Thyristor DC Drive Harmonics

TABLE 2  
HARMONIC CURRENTS PRESENT IN INPUT CURRENT TO A TYPICAL STATIC  
POWER CONVERTER IN PER-UNIT OF THE FUNDAMENTAL CURRENT [2]

Converter Pulses	Harmonic Order							
	5	7	11	13	17	19	23	25
6	0.175	0.110	0.045	0.029	0.015	0.010	0.009	0.008

Reference: Nosh Medora and Alex Kusko, "Power Harmonic Problems at a Plastic Extrusion Plant," *IEEE IAS Annual Conference*, October 1995

# Impedance Diagram --- 300 kvar Capacitor

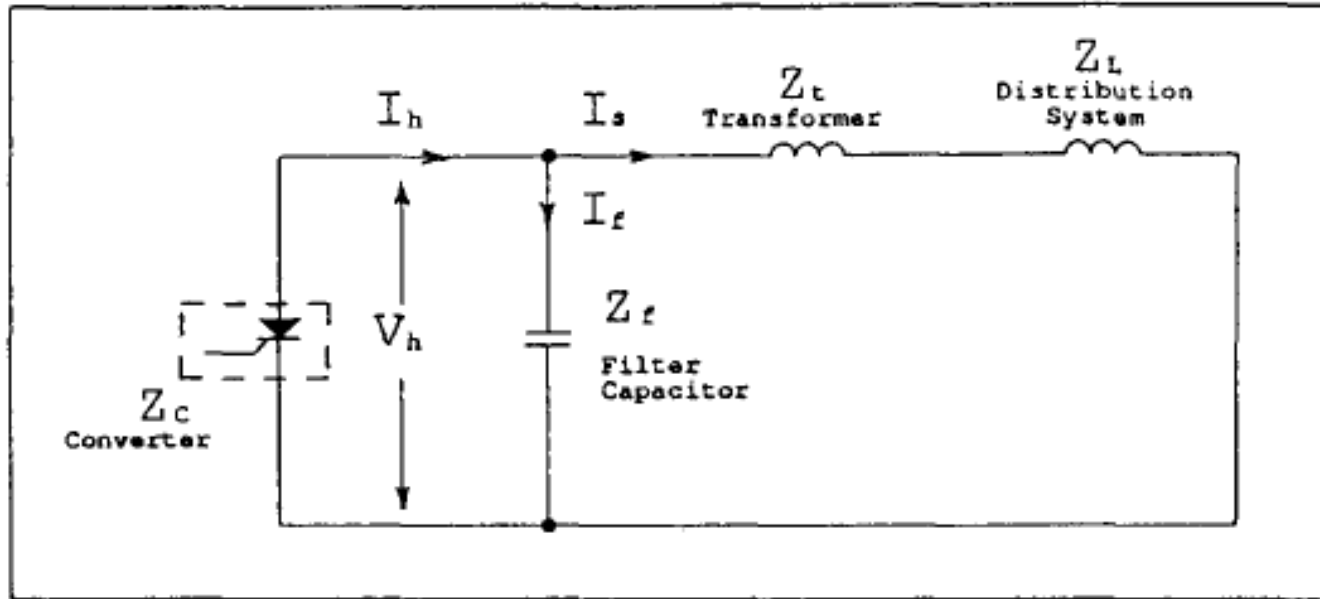


Fig. 3. Impedance Diagram of Power System [2]

Reference: Nosh Medora and Alex Kusko, "Power Harmonic Problems at a Plastic Extrusion Plant," *IEEE IAS Annual Conference*, October 1995



# Waveforms: Drive, Transformer, Capacitor Current. Fifth Harmonic Resonance

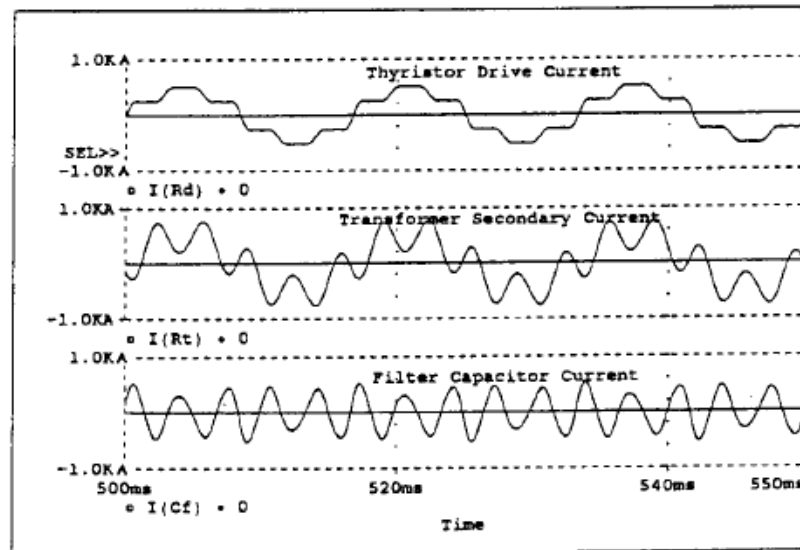


Fig. 7a. Thyristor Drive Current, Transformer Secondary Current, and Filter Capacitor Current vs. Time, No Series Reactor

Reference: Nosh Medora and Alex Kusko, "Power Harmonic Problems at a Plastic Extrusion Plant," *IEEE IAS Annual Conference*, October 1995

# Solutions to Harmonic Problem

- Do not install capacitors
- Install series reactor tuned to 5th harmonic
- Install larger, lower reactance, transformer
- Change drive to 12-pulse converter

Reference: Nosh Medora and Alex Kusko, "Power Harmonic Problems at a Plastic Extrusion Plant," *IEEE IAS Annual Conference*, October 1995

# Reactor Tuned to Fifth Harmonic: PSPICE Model

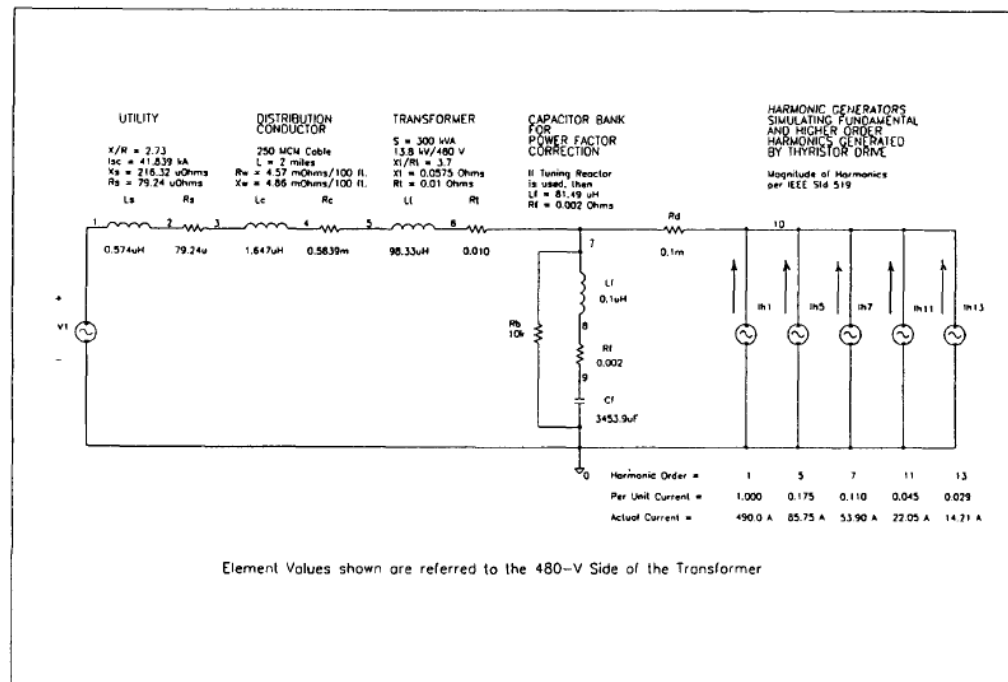


Fig. 4. One-Line Diagram of Electric Power System at Plastics Extrusion Plant

Reference: Nosh Medora and Alex Kusko, "Power Harmonic Problems at a Plastic Extrusion Plant," *IEEE IAS Annual Conference*, October 1995

# Waveforms: Drive, Transformer, Capacitor Current. Series Reactor Tuned to Fifth Harmonic

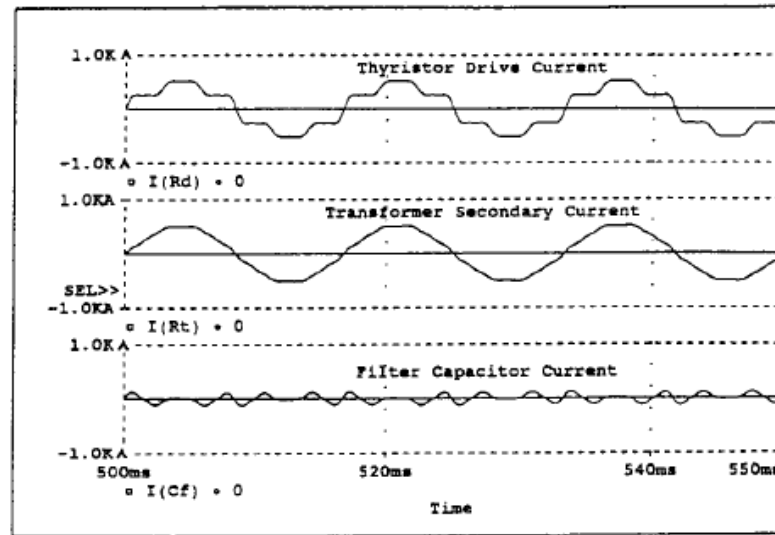


Fig. 7b. Thyristor Drive Current, Transformer Secondary Current, and Filter Capacitor Current vs. Time for Series Reactor Tuned to 5th Harmonic

Reference: Nosh Medora and Alex Kusko, "Power Harmonic Problems at a Plastic Extrusion Plant," *IEEE IAS Annual Conference*, October 1995

# Case Study, “Low Cost Power Monitoring of Diagnostic Imaging Systems”

- Require reliable and consistent power quality to insure proper operation
- Installed 40 “I-Sense” monitors to record power quality events
- Monitored three-phase voltages
- Printed out magnitude and duration of events on CBEMA format

Reference: D. A. Rush, “Low Cost Power Monitoring of Diagnostic Imaging Systems,,: *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004

# Case #1: Steady State Line Voltages

- Note: distortion of all three-phase voltages
- Corrected within facility

Case #1




Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004

# Case #2: Sags in Three-Phase Line Voltages


- Note: voltage sags in two of the phase voltages
- Problem on utility feeder

Case #2

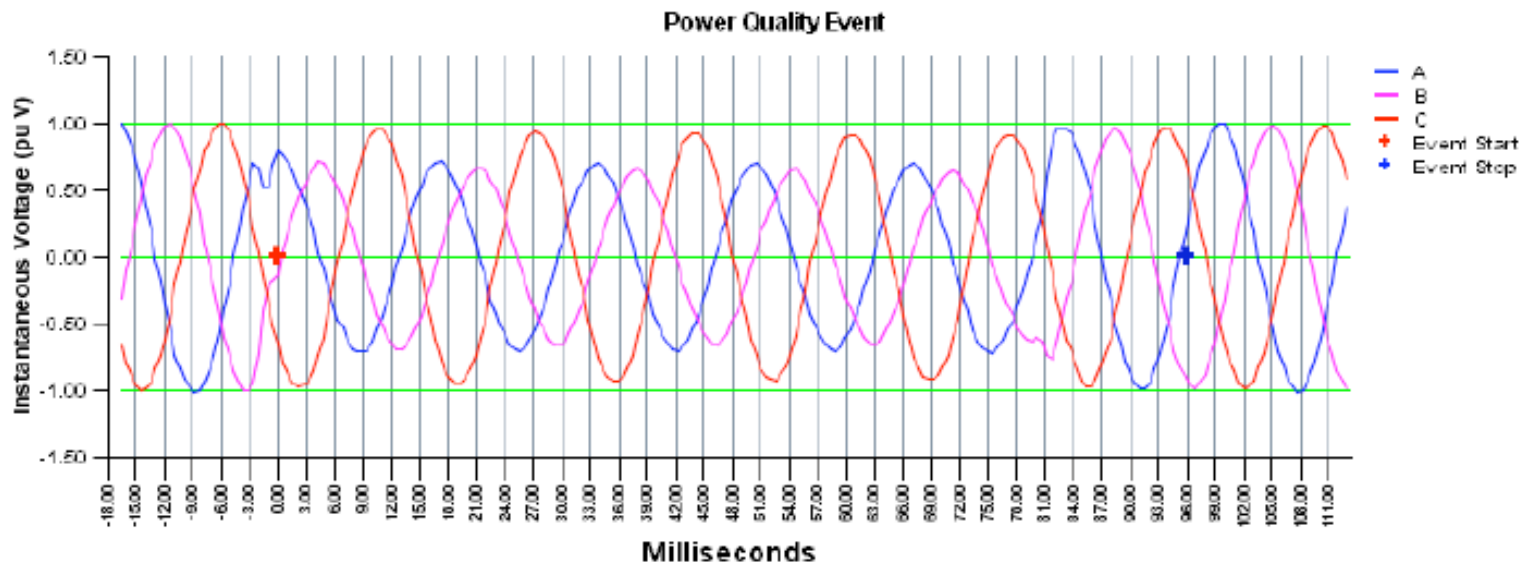

Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004

# Case #2: Outage Events on CBEMA Curve

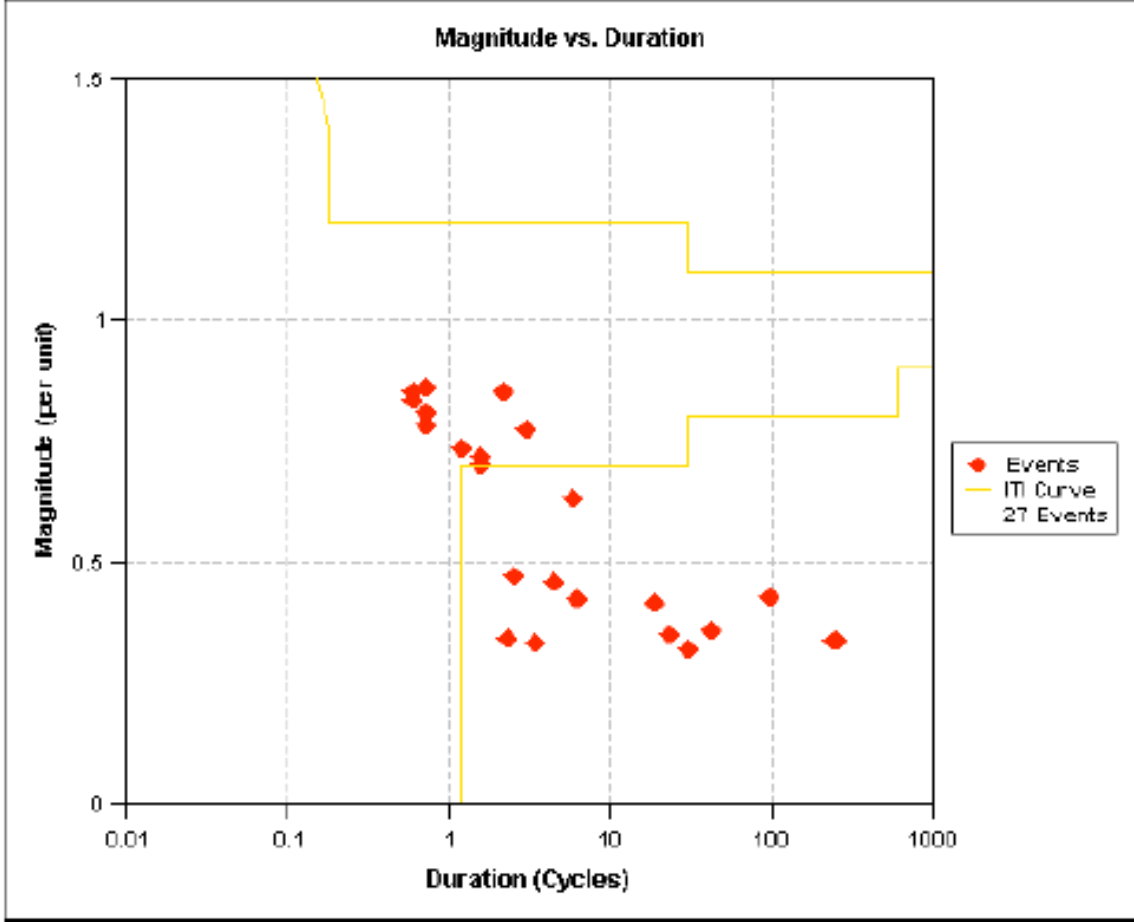


Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004



# Case #3: Sags in Three-Phase Line Voltages


- Note: utility distribution line fault cleared in 4 cycles

Case #3

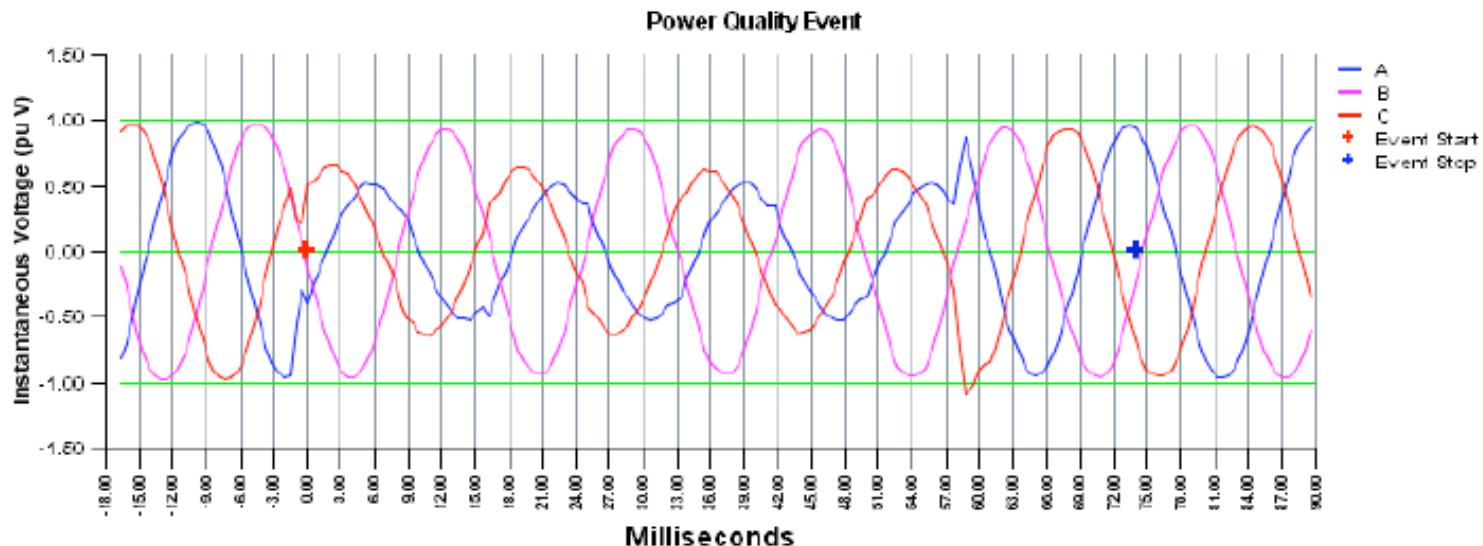

Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004

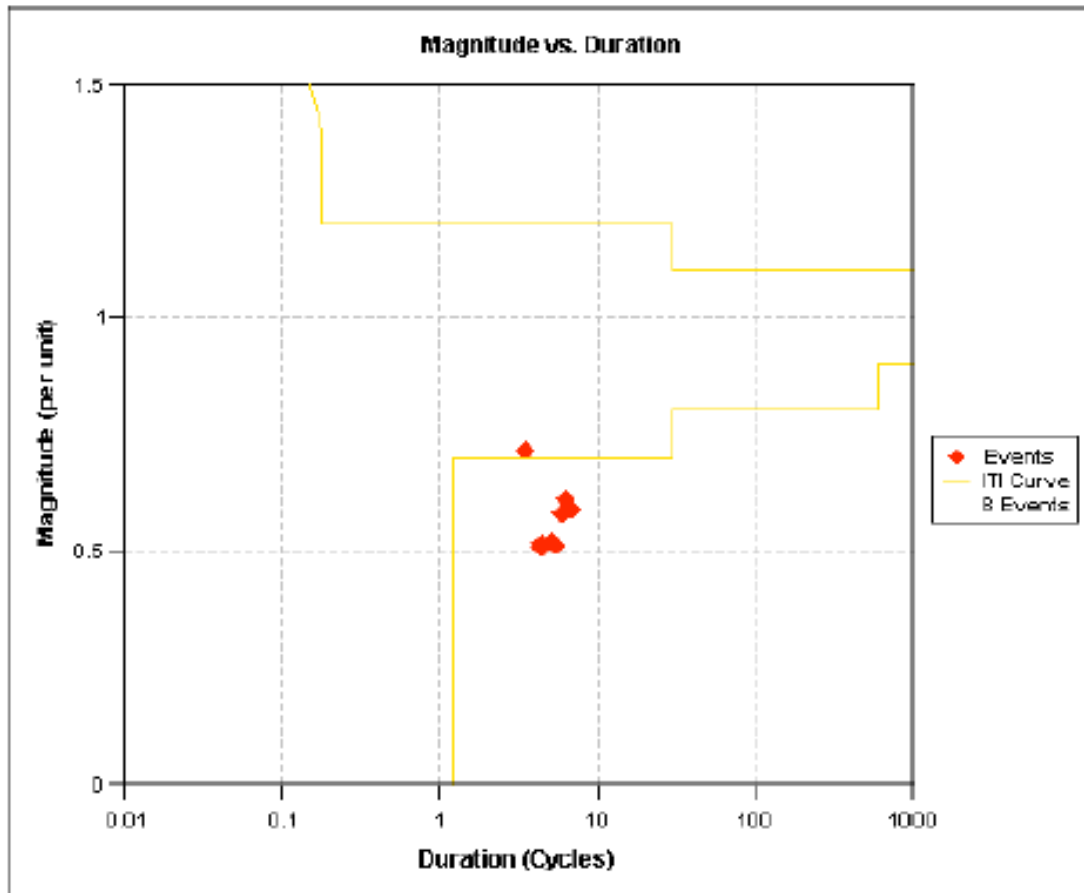
# Case #3: Outage and Clearing Events on CBEMA Curve



Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004
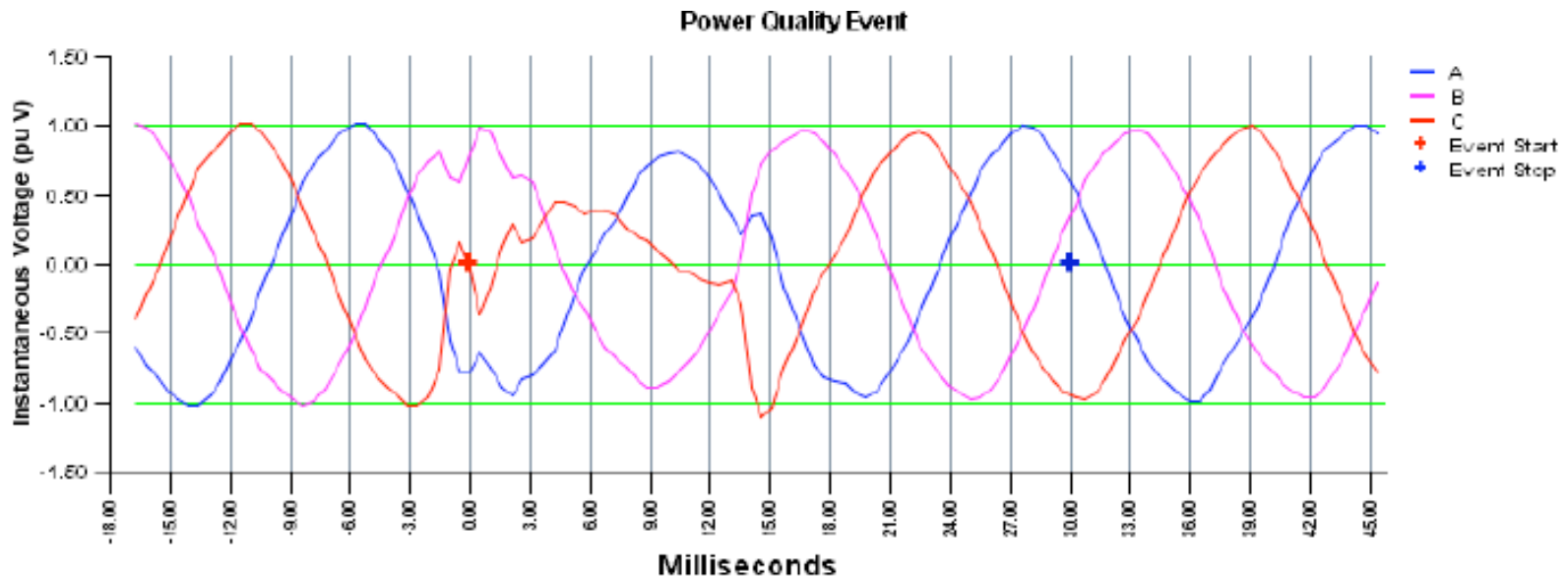
# Case #4: Capacitor Bank Switching


- Note: distortion of all three line voltages lasts about one cycle



Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004
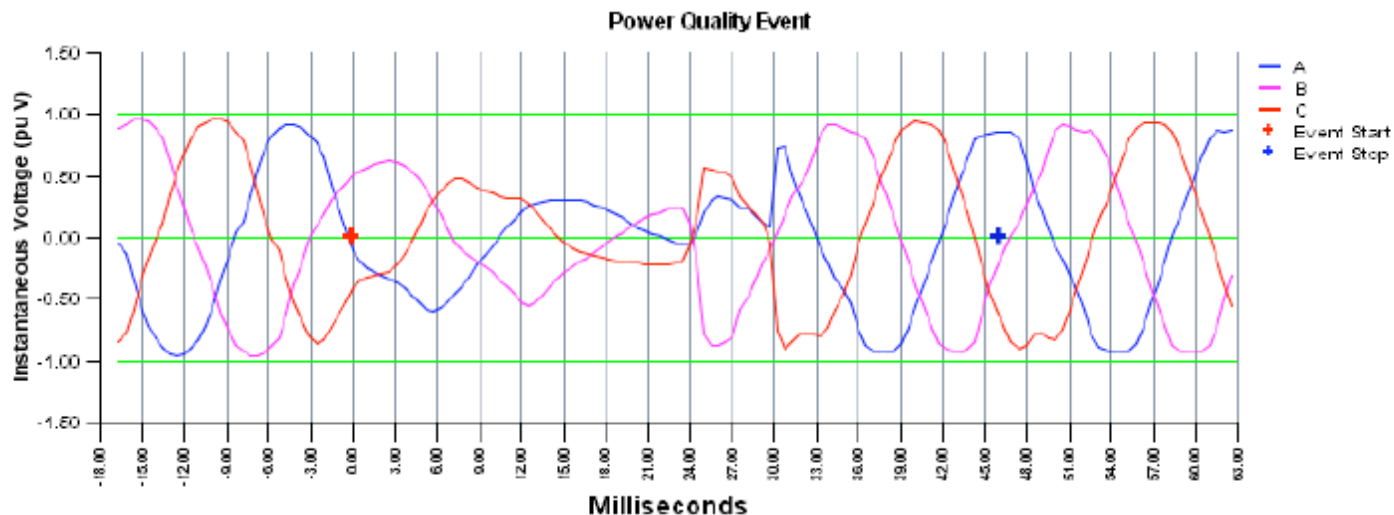
# Case #5: Transfer of Load From Utility to Backup Generator


- Note: Generator already up to speed and voltage
- Transfer takes two cycles. Voltages outside CBEMA curve. Generator voltage distorted.



Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004
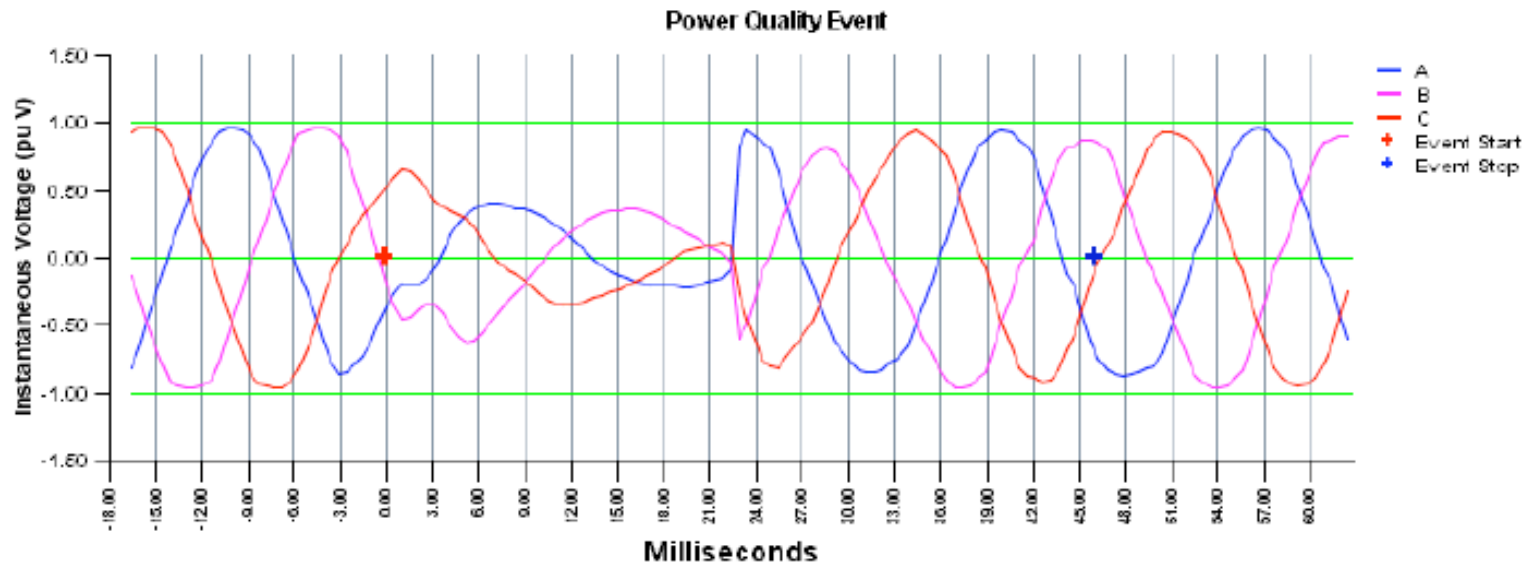
# Case #5: Transfer of Load From Backup Generator to Utility

- Note: transfer takes two cycles to achieve steady utility voltage




Reference: D. A. Rush, "Low Cost Power Monitoring of Diagnostic Imaging Systems,": *Power Quality Exhibition and Conference*, Chicago IL, November 16-18, 2004

# Effects of Harmonics on Equipment

- Adjustable speed drives (ASD)
- Capacitors
- Circuit breakers and fuses
- Conductors
- Electronic equipment
- Lighting
- Meters
- Protective relaying
- Rotating machines
- Telephone interference
- Transformers


Reference: "Report of the IEEE Task Force on the Effects of Harmonics on Equipment," *IEEE Transactions on Power Delivery*, April 1993, pp. 672-680

# Resonance: Model of Power System

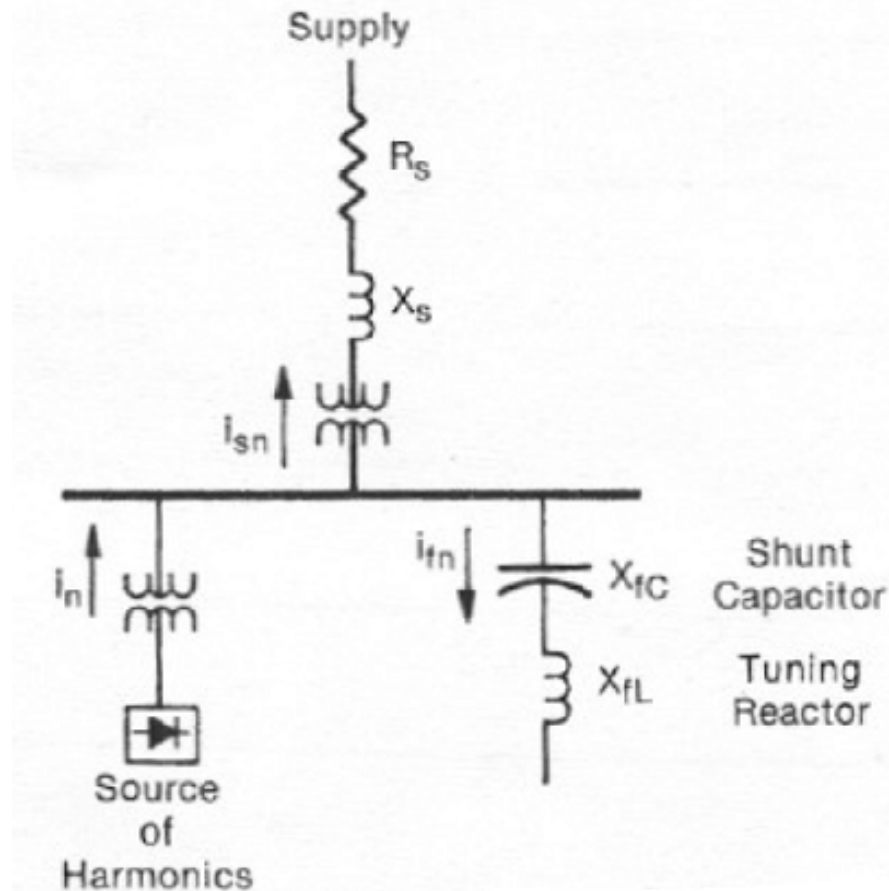

Reference: T. J. E. Miller, *Reactive Power Control in Electric Systems*, John Wiley, pp. 339

# Resonance Equivalent Circuit

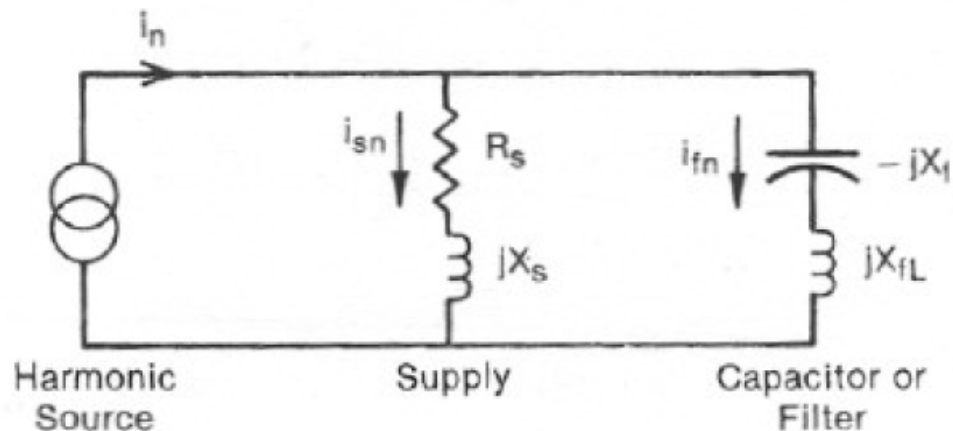

$$i_{sn} = \rho_s i_n$$

$$i_{fn} = \rho_f i_n$$


$\rho_s$  = supply distribution factor

$\rho_f$  = capacitor or filter distribution factor

Reference: T. J. E. Miller, *Reactive Power Control in Electric Systems*, John Wiley, pp. 339



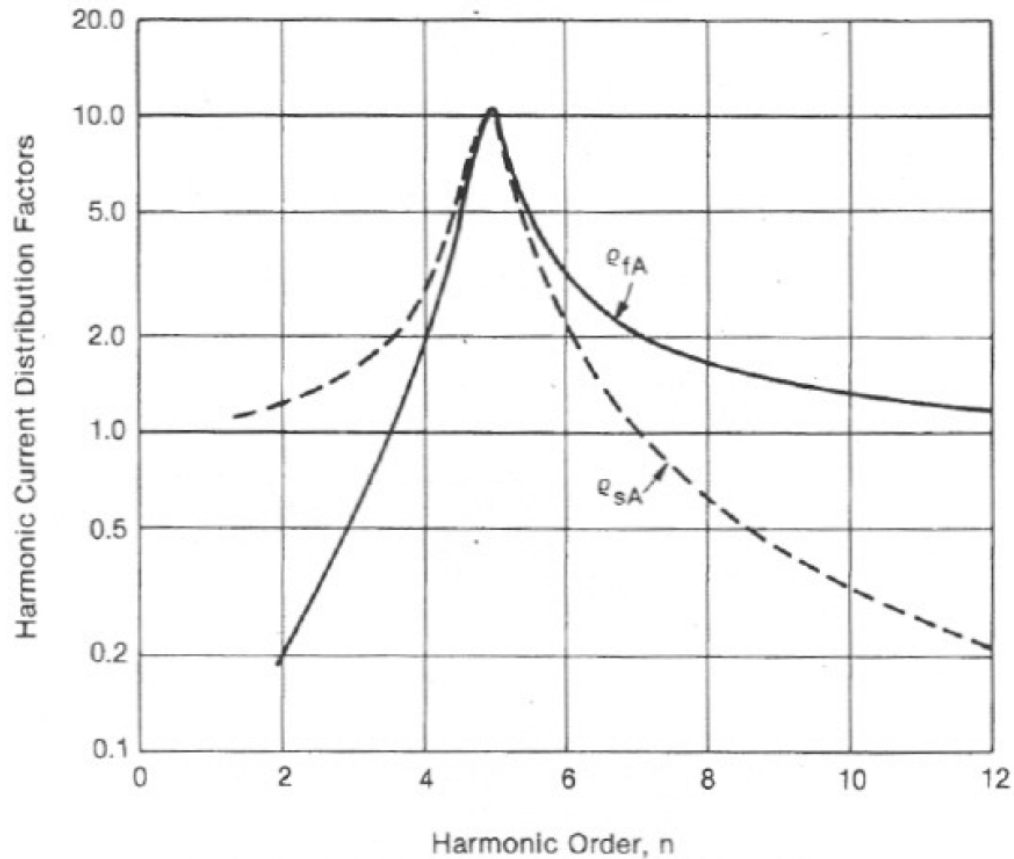
# Resonance: Distribution Factor, No Reactor



Reference: T. J. E. Miller, *Reactive Power Control in Electric Systems*, John Wiley, pp. 341
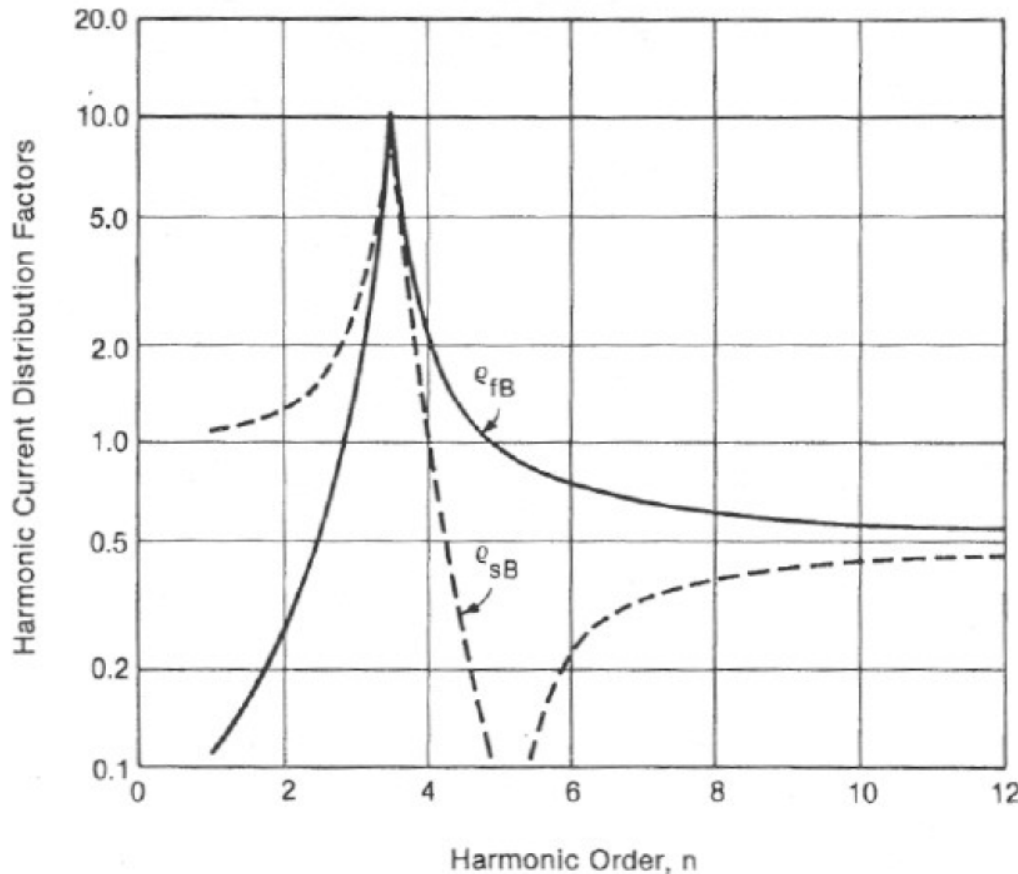
# Resonance: Distribution Factor, with Reactor



$$\rho_{fB} \rightarrow 1 \text{ at } n = 5$$
$$\rho_{sB} \rightarrow 0 \text{ at } n = 5$$

Reference: T. J. E. Miller, *Reactive Power Control in Electric Systems*, John Wiley, pp. 341